

1) The value of V_o is:

- a) 7.4 V b) 574 mV
c) 500 mV d) -6400 mV

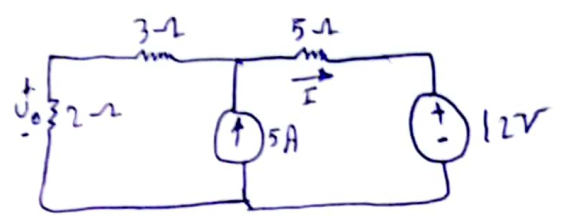


Fig. 1

2) The value of the current (i) in 5Ω is:

- a) -0.75 A b) 1.4 A
c) 1.3 A d) 0.7 A

3) The power absorbed by 3Ω resistor is:

- a) 5.23 W b) 6.46 W
c) 10.46 W d) 41.07 W

4) The Power absorbed by 12V voltage source is:

- a) 31.2 W b) 44.8 W
c) -15.6 W d) -44.8 W

Team
ZeroOne

Computer & Networks Engineers

Prob. 2: For question 5, 6 consider the current through a 1 mH inductor is $i(t) = 60 \cos 100t \text{ mA}$.

5) The terminal voltage across the inductor is:

- a) $-6 \sin 100t \text{ mV}$ b) $-6 \cos 100t \text{ mV}$
c) -9 V d) 6 mV

6) The Energy stored in the inductor is:

- a) $18 \sin^2(100t) \mu\text{J}$ b) $1.8 \cos^2(100t) \mu\text{J}$
c) $180 \mu\text{J}$ d) 18 mJ

11

Prob 3: For question 7, 8, 9, 10 consider the circuit shown in Figure 2.
The switch has been closed for a long time. At $t=0$, the switch is opened.

7) The initial current $i(t=0^+)$ is:

- a) 24 A b) 60 A
- c) 36 A d) 6 A

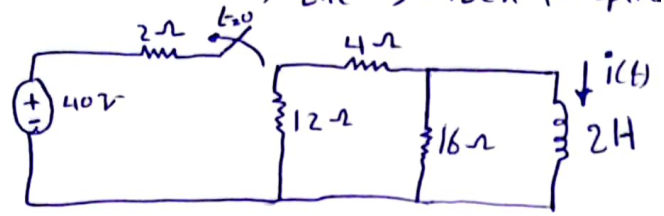


Fig. 2

8) The time constant of the circuit is:

- a) 120 s b) 250 ms
- c) 60 s d) 500 ms

9) The current in the inductor at $t=500$ ms is:

- a) 128.8 mA b) 0.812 A
- c) 606.5 mA d) 2.8 A

10) The final value of the voltage $v(t=\infty)$ across the inductor is:

- a) 0 V b) 36 V
- c) 24 V d) 12 V

prob. 4: Consider the circuit shown in figure 3. Use the Thevenin's theorem with respect to terminals (a-b)

- The Thevenin voltage is _____
- The Thevenin resistance is _____
- The current I is _____

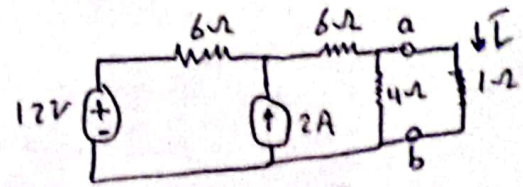


Fig 3

- what is the value of the load resistance that should be connected to the ab terminal to achieve maximum power transfer? _____

prob. 5: Consider the circuit shown in figure 4. And answer

- The value of α (damping factor) is: _____
- The value of ω_0 (resonant frequency) is _____
- The value of s_1 is _____
- The value of s_2 is _____
- The natural response $i(t)$ for $t > 0$ in general form is _____
- The initial inductor current $i(0)$ is _____
- The initial capacitor voltage $v(0)$ is _____


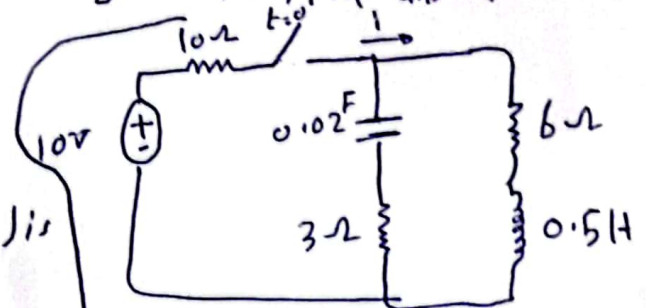


Fig. 4

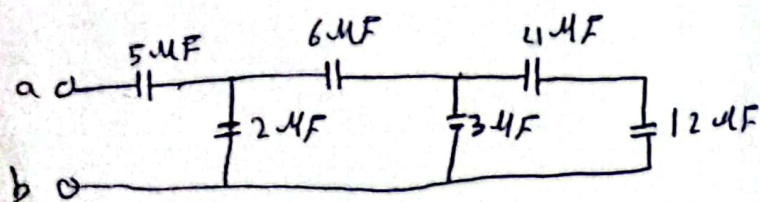prob 6: a) Refer to figure 5; the value of the equivalent capacitance is: _____



b) Refer to Figure 6; the value of the equivalent resistance is

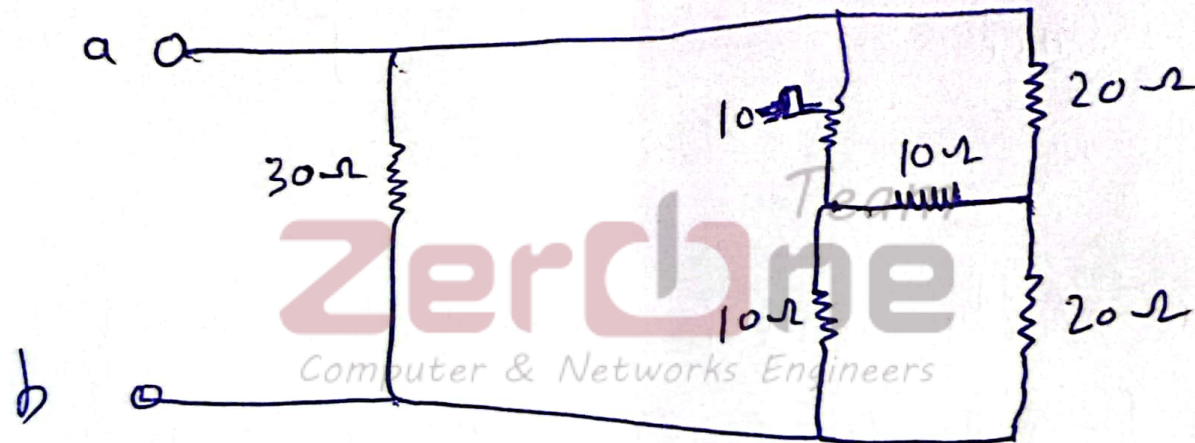


Fig. 6