



Note: Write all the required equations (without simplification) to solve the following problems, then find the final answer.


Prob. 1: Consider the circuit shown in Fig. 1,

1. The open circuit voltage between $a-b$ terminals (V_o), when the load impedance is disconnected, is:

$$(8 - j4) / (5 + j10) \quad I_5 \times 5 \Omega = V_o = 23.4 - j29.2 \text{ V}$$

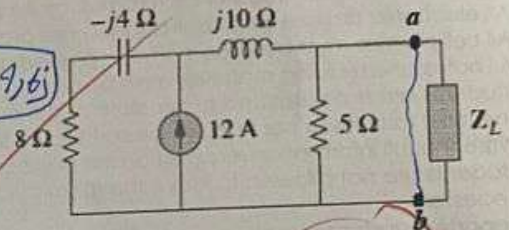2. The short circuit current (I_{sc}), when $a-b$ terminals are shorted is:

$$I_{sc} = \frac{V_L}{Z_L} \rightarrow \frac{96 + j48}{10j} = 4.8 - j9.6 \text{ A}$$



3. If the load impedance $Z_L = 8 + j6 \Omega$, The load current is:

$$V_L = V_o = 20 - j20 \text{ V}$$

Fig.1

Prob. 2: Consider the circuit shown in Fig. 2 and using mesh analysis method,

1. Write the two mesh equations, do not simplify:

$$\begin{aligned} I_1 &\rightarrow -40 \angle 30^\circ + j10 I_1 - 20j(I_1 - I_2) = 0 \\ I_2 &\rightarrow 40 I_2 + 50 \angle 0^\circ - 20j(I_2 - I_1) = 0 \end{aligned}$$

2. The current I_1 is: $-0.428 + j4.678 \text{ A}$

3. The current I_2 is: $0.785 + j0.607 \text{ A}$

4. The capacitor current, I_C , is: $81.42 \angle 4.26^\circ \text{ A}$

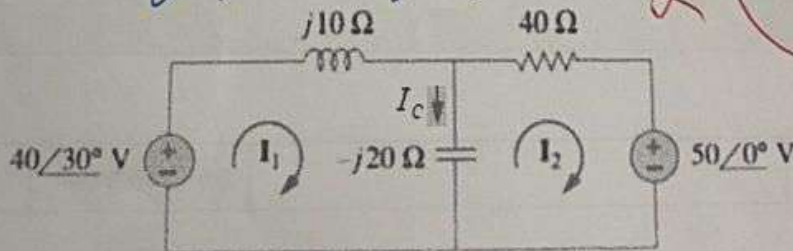


Fig 2

Consider the circuit shown in Fig. 3.

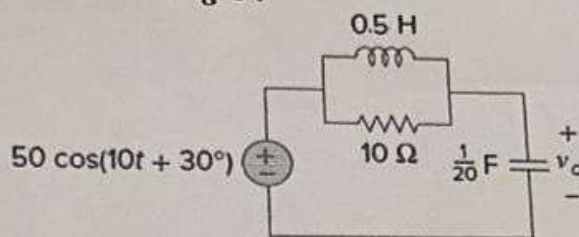


Figure 3

1. The equivalent admittance across the terminals of the source is:

$$Y = \frac{1}{Z} \rightarrow 0,25 - 0,25j$$

2. The voltage (V_0) is:

$$V_0 = I \times Z_C \rightarrow -1,15 - 34,15j$$

3. The current through 10Ω resistor in phasor domain is:

$$I_{10} = \frac{V_0}{Z_R} \rightarrow 5,24 + 5,91j$$

4. The total current lags the voltage of the voltage source by :

$$45^\circ \text{ degrees}$$