

Prob. 4: Consider the circuit shown where $V_x = 20V$ and $I_y = 4A$. Using *mesh method*.

a. Write all the required equations to find i_1 , i_2 , i_3 , and v_o (Do not simplify)

b. Solve to find i_1 , i_2 , i_3 , and v_o .

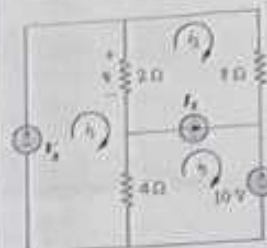


Figure 4

a.

~~i_1~~

$$8I_2 + 10 + 4(I_3 - I_1) - 2(I_2 - I_1) = -4$$

$$-2I_1 + 6I_2 + 4I_3 = -10 \Rightarrow \textcircled{1}$$

$$I_3 + I_3 = I_2$$

$$I_3 + 4 = I_2$$

$$I_2 - I_3 = 4 \Rightarrow \textcircled{2}$$

$$2(I_1 - I_2) + 4(I_1 - I_3) = -V_x$$

$$6I_1 - 2I_2 - 4I_3 = -20 \Rightarrow \textcircled{3}$$

Computer & Networks Engineers

b.

$$i_1 = -6.75A$$

$$i_2 = -0.75A$$

$$i_3 = -4.75A$$

$$2(I_1 - I_2) = -12V$$

Prob. 1: Consider the circuit shown where $V_S = 10V$.

a. Using voltage divider, find V_x and V_{AB} .

b. Using Ohm's law, find I_S and I .

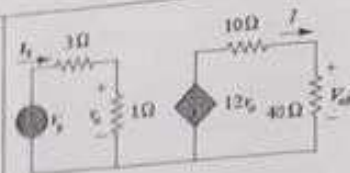


Figure 1

a.

$$V_x = 7.5V$$

$$V_{AB} = -72V$$

b.

$$I_S = \frac{V_S}{R_{eq}} = \frac{30}{4} = 7.5A$$

$$I = \frac{-12V_0}{R_{eq}} = \frac{-40}{50} = -1.8A$$

Prob. 2: Consider the circuit shown where $R = 14\Omega$.

a. Find the equivalent resistance between the a-b terminals.

b. When the voltage between the a-b terminals is 84 V, find the current I and the voltage V_x .

c. When $I = 10A$, using current division, find the current through the 30Ω resistance.

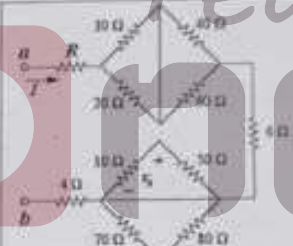


Figure 2

a.

$$R_{eq} = 61.33\Omega$$

b.

$$I = \frac{V}{R_{eq}} = \frac{84}{61.33} = 1.367A$$

$$V_x = 0V \text{ (short circuit)}$$

c.

$$I_{30} = \frac{V}{R_{30}} = \frac{24}{30} = 2.8A$$

Prob. 3:

(a) The charge transferred through a circuit element is given by $q(t) = 6t^2 + 6t$ C. Calculate the current entering the element at instant $t = 10ms$.

$$i(t) = 126A$$

(b) If a load draws 1kW when connected to a 230 V source, then the resistance of the load (R_L) is

$$R_L = 15.16\Omega$$

Prob. 5: Consider the circuit shown where $I_s = 2A$. Using nodal method:

a. Write all the required equations to find v_1 , v_2 , v_3 , and I_o (Do not simplify)

b. Solve to find v_1 , v_2 , v_3 , and I_o .

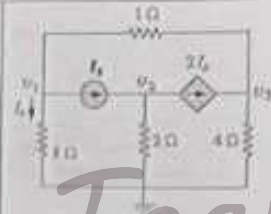


Figure 5

$$I_o + I_s + \frac{v_1 - v_3}{1} = 0$$

$$I_o + v_1 - v_3 = -2$$

$$\frac{7v_1}{8} - v_3 = -2 \Rightarrow \textcircled{1}$$

$$-I_s + \frac{v_2}{2} + 2I_o = 0$$

$$2I_o + \frac{v_2}{2} = 2$$

$$\frac{7v_1}{8} + \frac{v_2}{2} = 2 \Rightarrow \textcircled{2}$$

$$\frac{v_3}{4} + \frac{v_2 - v_1}{1} - 2I_o = 0$$

$$-v_1 + \frac{5v_2}{4} - 2I_o = 0$$

$$\frac{-11v_1}{4} + \frac{5v_2}{4} = 0 \Rightarrow \textcircled{3}$$

b.

$$v_1 = 1.5V \quad ; \quad v_2 = -1.28V$$

$$v_3 = 3.32V \quad ; \quad I_o = \frac{1.5}{8} = 0.1875A$$