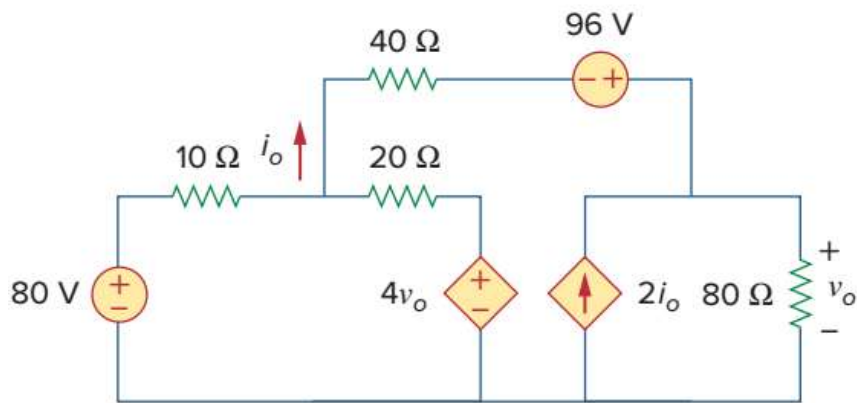



Q1: Find the values of v_o and i_o , Show equations & steps.

(12 marks)



Q2: For the shown figure, find the following:


(8 marks)

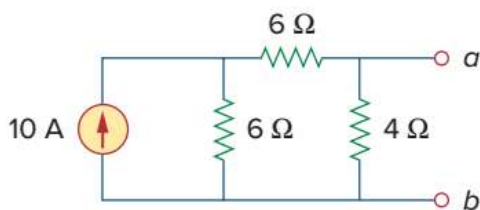

1. Thevenin's equivalent circuit.
2. Norton's equivalent circuit.

Q3: Write ∇ -Y transformation equations in figure.

(5 marks)

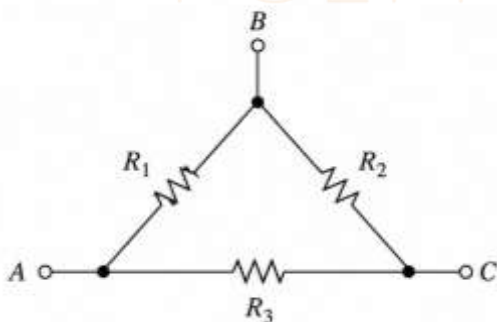

Q4: Prove that The maximum power transferred is $\frac{V_{Th}^2}{4R_{Th}}$.

(5 marks)

ملاحظة: بعض القيم في الامتحان كانت مختلفة في السؤالين 1 و 2، لكن نفس الفكرة للسؤال.