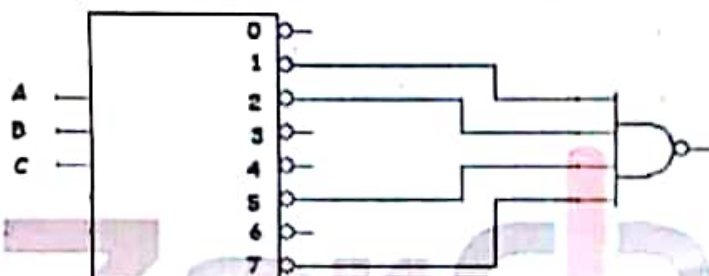




Select the correct answer, from options (a,b,c,d) to the following questions.
(5marks)

	1	2	3	4	5
Ans.	a	d	d	a	d

1. The function that can be implemented from the following decoder is:
 $F(A,B,C) = \dots\dots\dots$



AND $\rightarrow x$

- (a) $\Sigma(1,2,5,7)$ b- $\pi(1,2,5,7)$ c- $\Sigma(0,3,4,6)$ d- a and b

2. How many 4-bit parallel adders would be required to add two binary numbers each representing decimal numbers up to three hexadecimal digits?

- a- 1 b- 2 c- 3 d- 4

3. You can implement the overflow bit using

- a- AND gate b- OR gate c- XOR gate d- XNOR gate

4. To multiply two binary numbers, the multiplier = 4 by the multiplicand = 5, You will need:

- (a) 20 AND gates b- 9 AND gates c- 15 AND gates d- 16 AND gates

5. To multiply two binary numbers, the multiplier = 4 by the multiplicand = 5, You will need:

- a- Two 4-bit adders
b- Two 5-bit adders
c- Three 4-bit adders
d- Three 5-bit adders

$$A: A_3 A_2 A_1 A_0$$

$$B: B_4 B_3 B_2 B_1 B_0$$

$$A_3 B_4 A_2 B_3 A_1 B_2 A_0 B_1 A_0 B_0$$

$$A_1 B_4 A_1 B_3 A_1 B_2 A_1 B_1 A_1 B_0$$

$$A_2 B_4 A_2 B_3 A_2 B_2 A_2 B_1 A_2 B_0$$

$$A_3 B_4 A_3 B_3 A_3 B_2 A_3 B_1 A_3 B_0$$

$$\begin{array}{r} 16^2 \\ 16 \\ 16 \\ \hline 96 \\ 960 \\ \hline 1056 \end{array}$$

BCD

Q2) Design a 4-bit adder which implement the following conditions.

A- If the addition result is ≥ 12 or a carry out then number 3 must be added to the result, Else add zero.


Q3) Implement the function $F_{ABCD} = \sum(0, 3, 6, 7, 8, 11, 14, 15)$ using Multiplexer, Use inputs A, C, D as select lines.

Q4) Design the following function: $F(A, B, C, D) = (\bar{A}B + AC)\bar{D}$ using:

- a) NAND gates only.
- b) NOR gates only.


Timer

Q2:

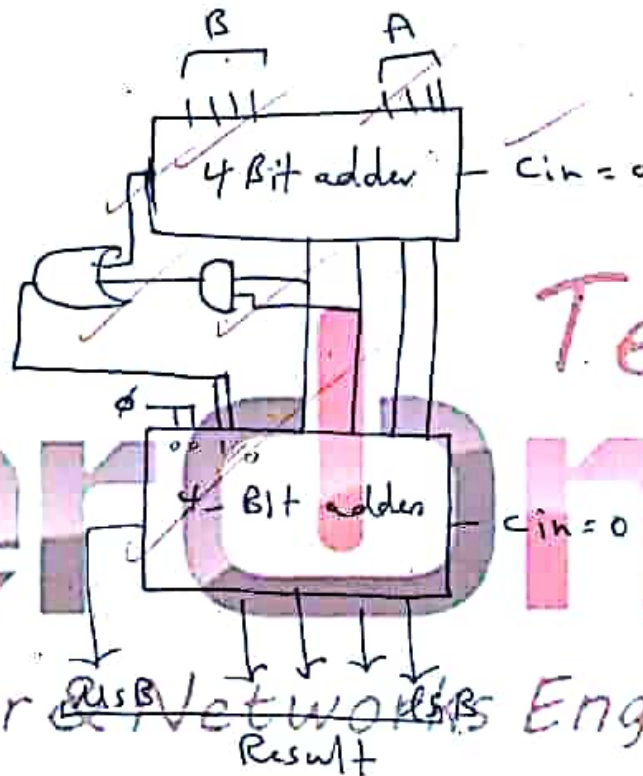

Computer & Network Engineers

Q3:

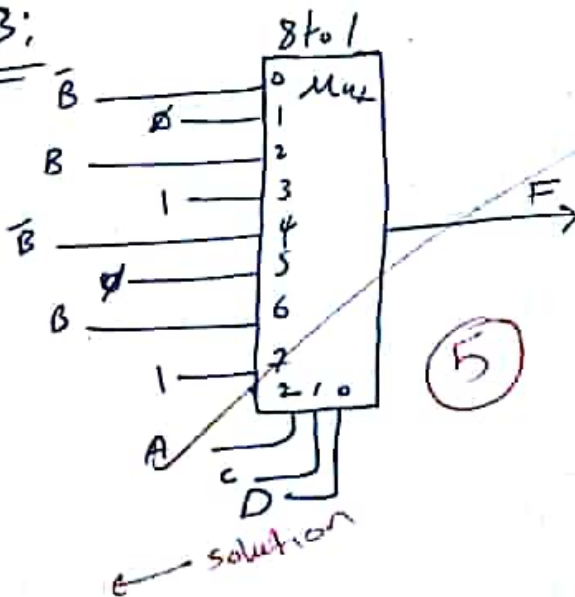

$$\begin{aligned} 000 &\rightarrow \bar{B} \rightarrow 1 (\checkmark) \\ 001 &\rightarrow \bar{B} \rightarrow 1 (\checkmark) \end{aligned}$$

Q4: $F = \sum(4, 6, 10, 14)$

a) Nand $\rightarrow$ sop

F


Using gates $\rightarrow$ SOP
 $F = \Sigma(4, 6, 10, 14)$

CD \ AB	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	0	0	1	0
10	0	1	0	1

$$F = \bar{A} B \bar{D} + A C \bar{D}$$

$$F = \overline{\bar{A} B \bar{D} \cdot A C \bar{D}}$$

2.5

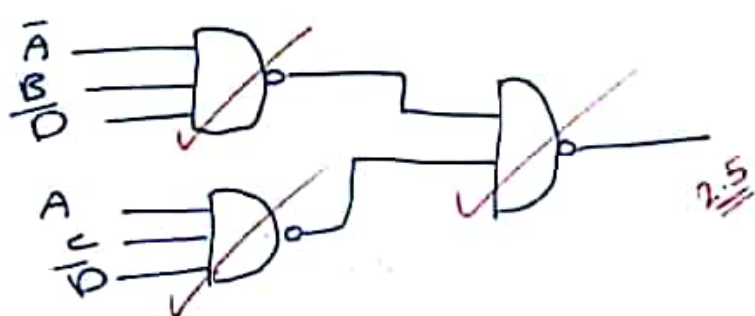

b) NOR Gates only:-

min term
 make:- 0: A
 1: A-bar

$$F = \bar{K}(0, 1, 2, 3, 5, 7, 8, 9, 11, 12, 13, 15)$$

CD \ AB	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	0	0	1	0
10	0	1	0	1

$$F = \bar{A} \bar{B} + \dots$$


$$F = (\bar{A} + \bar{B}) \cdot (\bar{D}) \cdot (A + \bar{C})$$

$$F = (A + B) \cdot (\bar{D}) \cdot (\bar{A} + \bar{C})$$



$$F(\text{max}) = 0 = (0+0) \cdot (0) \cdot (1+0) = 0$$

$$F = \overline{(A + B) \cdot (\bar{D}) \cdot (\bar{A} + \bar{C})}$$
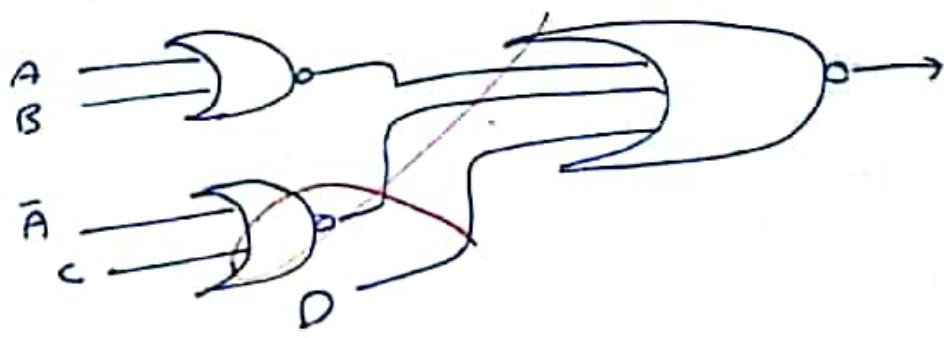
$$F = \overline{(A + B)} + \overline{(\bar{D})} + \overline{(\bar{A} + \bar{C})}$$



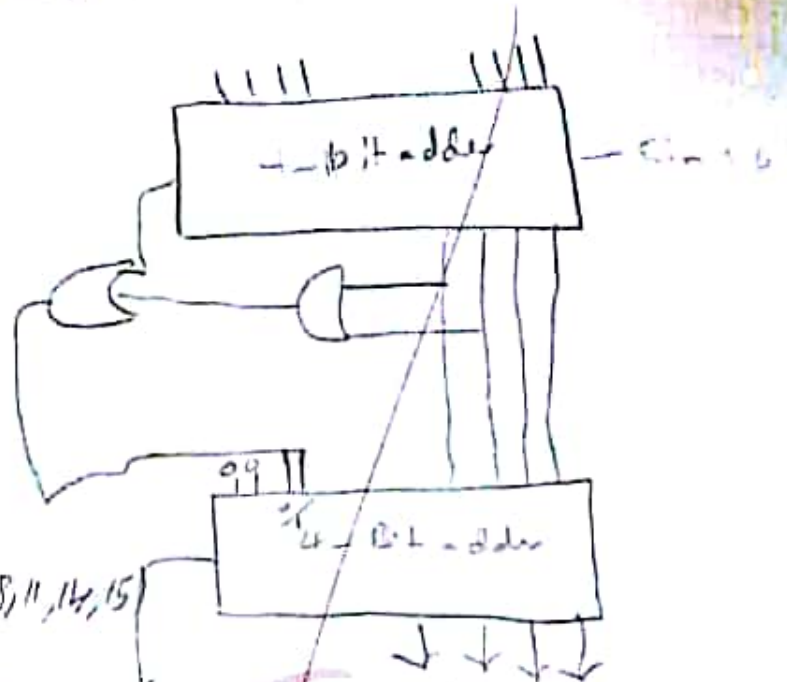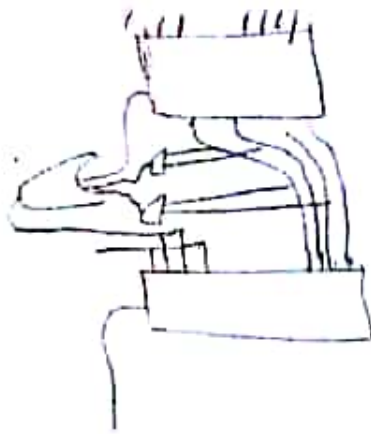Add. in (7=12) or a carry out the number? ^{add}
else add zero.



Q3: $F(A, B, C, D) = \Sigma(0, 3, 6, 7, 8, 11, 14, 15)$

Q3) $A < D \rightarrow C.S$

$\bar{B} @ 1, 2, 3, 8, 9, 10, 11$

$B @ 4, 5, 6, 7, 12, 13, 14, 15$

$B \oplus B \oplus 1 \oplus 0 \oplus B \oplus 1$

$0 \oplus 1 \oplus 1 \oplus 0 \oplus 0 \oplus 1$

Q4: $F(A, B, C, D) = (\bar{A}B + AC) \cdot \bar{D}$

a) Nand gates.

b) NOR gates.

$F = \bar{A}B \bar{D} + AC \bar{D}$

$0100 \quad 1010$

$0110 \quad 1110$

$F = \Sigma(0, 1, 2, 3, 5,$

$F = \Sigma(4, 6, 10, 14)$

Nand $\rightarrow$ sop

$0100 \quad 0110 \quad 1010 \quad 1110$

$F = \bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} B \bar{C} \bar{D} + A \bar{B} C \bar{D} + A B C \bar{D}$

	B	F
0	0	1
1	0	0
2	0	0
3	0	1
4	1	0
5	1	0
6	1	1
7	1	1
8	0	1
9	0	0
10	0	0
11	0	1
12	1	0
13	1	0
14	1	1
15	1	1

Computer Networks Engineers