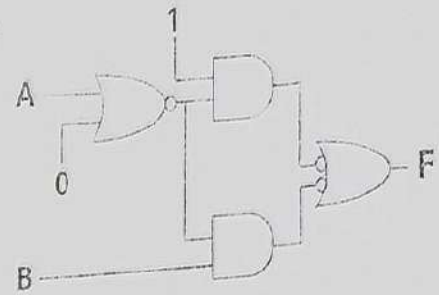




Q. # 1: Answer the following Multiple-choice questions: [10 x 1pt]

The output **F** of the combinational circuit shown to the right is:

- A. $\bar{A} + B$ B. 1 C. $A + \bar{B}$ D. $\bar{A} + \bar{B}$



2- The range of signed decimal numbers that can be represented by 9 bits is:

- A. -256 to +255 B. -128 to +128 C. -64 to +63 D. None of the above

3- The Hexadecimal representation of $(45.0625)_{10}$ is:

- A. $(2C.4)_{16}$ B. $(2D.02)_{16}$ C. $(2E.04)_{16}$ D. None of the above

4- In 16-bit 2's complement representation, the decimal number -34 is:


- A. 0000000000100010 B. 1111111111011101
C. 1111111111011110 D. None of the above

5- The result of $(F0ACD472)_{16} + (89D34FA9)_{16}$ is:

- A. $(17A80231B)_{16}$ B. $(17B80241B)_{16}$
C. $(17A80251B)_{16}$ D. None of the above

6- The combinational circuit shown in the right is:

- A. 1
B. $\bar{A}$
C. 0
D. $\bar{B}$

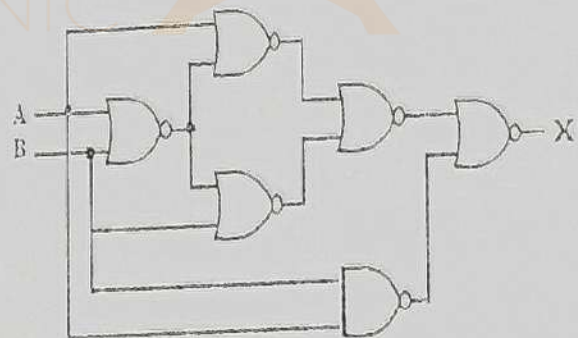

7- The equivalent SOP canonical form for the following logical expression

$$F(A, B, C) = AB + C \text{ is:}$$

- A) $F(A, B, C) = ABC + \bar{A}BC + A\bar{B}C + \bar{A}\bar{B}C$
B) $F(A, B, C) = ABC + A\bar{B}C + \bar{A}\bar{B}C + AB\bar{C}$
C) $F(A, B, C) = ABC + \bar{A}BC + A\bar{B}C + \bar{A}\bar{B}C + AB\bar{C}$
D) None of the above



Using 7-bit signed numbers (two's complement), which of the following decimal additions causes overflow?

- A. $45 + 13$
 C. $-32 + -33$
 B. $-24 + 15$
 D. None of the above

9- Simplified form of the Boolean expression $(X + Y + XY)(X + Z)$ is:

- A) $X + Y + Z$ B) $XY + YZ$ C) $X + YZ$ D) None of the above

10- If $F(x, y, z, w) = \pi(0, 3, 5, 7, 8, 9, 10, 15)$, the complement of F ($\bar{F}$) is:

- A. $\pi(1, 2, 4, 6, 11, 12, 13, 14)$ B. $\pi(1, 2, 4, 6, 11, 12, 10, 14)$
 C. $\sum(0, 3, 5, 7, 8, 9, 10, 15)$ D. None of the above

*** Write the correct answers to problem # 1 in the table below:

Problem#2: Find all possible most simplified SOP (Sum of Products) expressions for


$$F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 8, 10, 15)$$

together with the don't care conditions $d(A, B, C, D) = \sum(7, 13, 14)$

You must show all steps, including the drawing of the cells and grouping cells together, etc. [8pts]



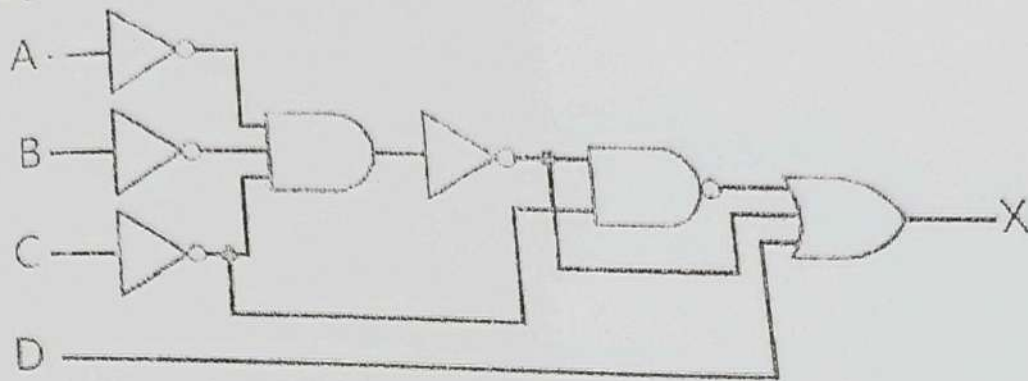Problem # 3: Based on the below combinational circuit, find the minimal form of X function using Boolean algebra rules. [6pts]



Spark


POLYTECHNIC





University
Item # 4.

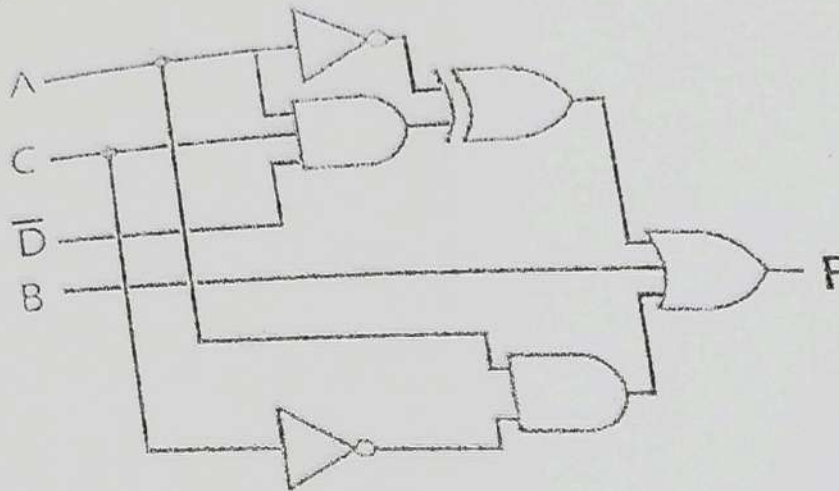Implement the combinational circuit below using only NAND gates. [6pts]



Spar

POLYTECHNIC



Good Luck