



Al-Qadisiyah Applied University
Faculty of Engineering Technology
Department of Electrical Engineering

Electronics I
Final Exam 24-4-2024
1st Semester 2023/2024


Student Name: أحمد يوسف طالب
أبو زيد

Instructor Name:

1. Select the correct answer for the following questions:

The value of α when $\beta = 100$ is
a. 1.01 b. -101 c. 0.99 d. -9.9

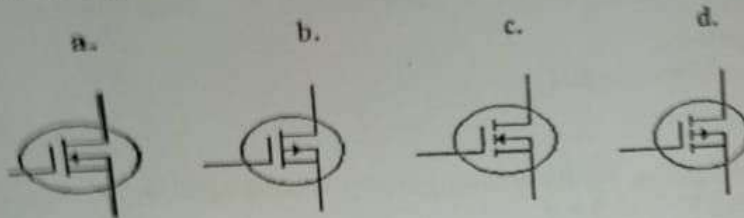2. Which figure represents a p-channel E-MOSFET?



3. In BJT small signal model, the h_{21} parameter unit in hybrid equivalent model is.....
a. Ohms. b. Ampere. c. Volt. d. Unitless.

4. In BJT small signal model, the h_{11} parameter in hybrid equivalent model is calculated by
a. Making an open circuit at the input terminals.
b. Making an open circuit at the output terminals.
c. Making a short circuit at the output terminals.
d. Making a short circuit at the input terminals.

5. Using the data sheet for a BJT transistor, the parameter h_{FE} represents
a. α_{ac} b. β_{dc} c. β_{ac} d. α_{dc} e. None of them.


3. In BJT small signal model, the h_{21} parameter unit in hybrid equivalent model is.....
a. Ohms. b. Ampere. c. Volt. d. Unitless.

4. In BJT small signal model, the h_{11} parameter in hybrid equivalent model is calculated by
a. Making an open circuit at the input terminals.
b. Making an open circuit at the output terminals.
c. Making a short circuit at the output terminals.
d. Making a short circuit at the input terminals.

5. Using the data sheet for a BJT transistor, the parameter h_{FE} represents
a. α_{ac} b. β_{ac} c. β_{dc} d. α_{dc} e. None of them.

6. The best BJT configuration that provides the best Q-point stability with single-polarity supply voltage is.....
a. Emitter follower. b. Collector-feedback. c. Voltage-divider. d. Fixed-bias.

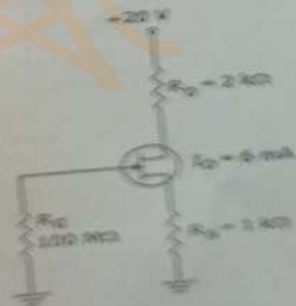7. Using the figure shown below, the value of V_s is equal to.....
a. 6 V. b. 8 V. c. 20 V. d. 2 V e. None of them.




8. In JFET semi-conductor, when V_{DS} is greater than V_P , the JFET has a characteristic of

- a. Voltage source. b. Current source. c. Ohmic region. d. None of them.

9. For the circuit shown below of collector characteristics, the value of β_{ac} for $V_{CE} = 15V$ and $I_B = 30 \mu A$ is equal to

- a. 160 b. 100 c. 50 d. 400.

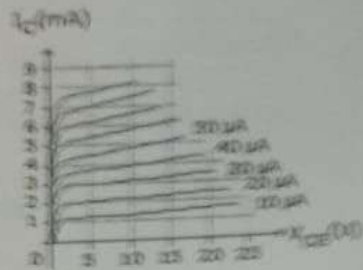


10. Which of the following is not correct about FET compared to BJT?

- a. FET is smaller size than BJT.
b. FET has a higher input impedance.
c. FET has Less temperature stability than BJT.
d. None of the above.

10. Which of the following is not correct about FET compared to BJT?
- FET is smaller size than BJT.
 - FET has a higher input impedance.
 - FET has Less temperature stability than BJT.
 - None of the above.

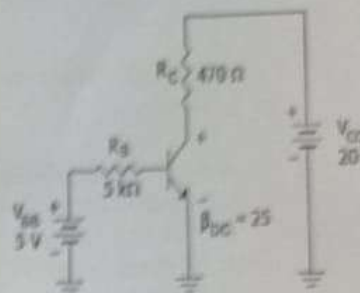11. The collector-emitter voltage V_{CE} for the following configuration is equal to.....
- 19.3 V
 - 9.2 V
 - 0.7 V
 - 9.9 V



12. In Shockley's equation for FET, the controlled variable that relates I_D and V_{GS} is.....
- I_{DSS}
 - V_P
 - I_D
 - V_{GS}


13. For a FET transistor, the I_{DSS} for $V_{GS} = -4.5$ V, $V_P = -8$ V, and $I_D = 6.12$ mA is
- 32 mA
 - 16 mA
 - 64 mA
 - 8 mA

14. The data sheet for E-MOSFET is given below. For $V_{GS}(\text{Th}) = 3$ V, the parameter k of MOSFET is.....

ON CHARACTERISTICS				
Gate Threshold Voltage ($V_{GS} = 10$ V, $I_D = 10 \mu\text{A}$)	$V_{GS}(\text{Th})$	1.0	5	V
Drain-Source On-Voltage ($I_D = 2.0$ mA, $V_{GS} = 10$ V)	$V_{DS}(\text{on})$	-	1.0	V
On-State Drain Current ($V_{GS} = 10$ V, $V_{DS} = 10$ V)	$I_{D}(\text{on})$	3.0	-	mA

- 6.17 mA/V²
- 6.17 V²/mA
- $0.061 \cdot 10^{-3}$ A/V²
- $0.061 \cdot 10^{-3}$ V²/A

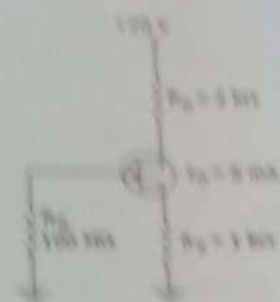14. For the following circuit, the value of V_{CE} is
 a. 2 V b. 4 V c. 2 V d. 24 V



15. For BJT transistor, the base-emitter junction in saturation region is
 a. Forward biased b. Reverse biased c. Ohmic region d. None of them

16. Assume that an electronic technician needs to design a circuit that makes the Q-point of the load line of the following circuit is going up toward the V_{CE} , then the value of should be
 a. R_B increased b. R_B increased c. R_B decreased d. R_B decreased e. R_B increased




17. The following BJT configuration is called configuration.
 a. Common base b. Common emitter c. Common base d. None of them




18. In a pnp transistor, the current carriers are
 a. Accepted ions b. donor ions c. electrons d. holes

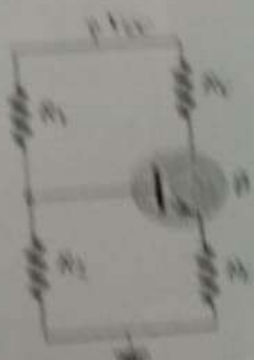19. For the following BJT configuration, the base current is
 a. $I_B = \frac{V_{CE} - V_{BE}}{R_{B1} + (1 + \beta)R_E}$ b. $I_B = \frac{V_{CE} - V_{BE}}{R_{B1} + (1 + \beta)R_E}$ c. $I_B = \frac{V_{CE} - V_{BE}}{R_{B1} + (1 + \beta)R_E}$ d. $I_B = \frac{V_{CE} - V_{BE}}{(1 + \beta)}$



Q2. For the given circuit below, if $V_{GS(off)} = -8\text{ V}$, $I_{DSS} = 16\text{ mA}$, and $C = 2\text{ }\mu\text{F}$, answer the following:

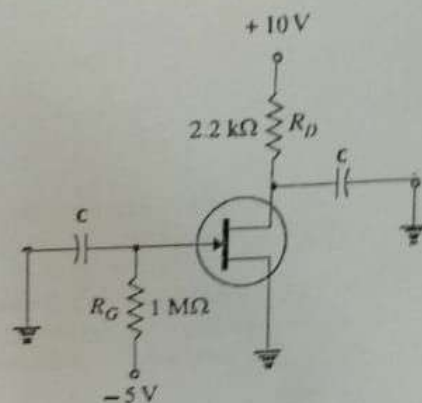1. What is the type of this transistor?
2. What is the name of this configuration?



4. What is the value of I_o .

5. What is the value of V_{DS} ?

Multiple Choice Answers of Question 1:

[illegible][illegible]