



Al-Balqa' Applied University
Faculty of Engineering Technology
Electronics I
Dr. Majed Dwairi

Mid Exam
2022/2023

جامعة البلقاء التطبيقية
كلية الهندسة التكنولوجية
Time: 50 min.
/11/2022

التخصص : هندسة حاسوب

اسم الطالب : المثنى خا لرا الطو

1- Each atom in a silicon crystal has:

- a- four valence electrons
- b- four conduction electrons
- ☒ c- eight valence electrons, four of its own and four shared
- d- no valence electrons because all are shared with other atoms

2- When a voltmeter is placed across a forward-biased diode, it will read a voltage approximately equal to:

- a- the bias battery voltage
- ☒ c- the diode barrier potential
- b- 0 V
- d- the total circuit voltage

* For forward bias for the silicon diode given $I_D = 4 \text{ mA}$ at 0.58 V answer the question (3 and 4)

3- the ac resistance at given current equal

- a- 6.5Ω
- ☒ b- 13Ω
- c- 145Ω
- d- 290Ω

4- The dc resistance at this current level is

- a- 6.5Ω
- b- 13Ω
- ☒ c- 145Ω
- d- 290Ω


5- The depletion region consists of

- a- nothing but minority carrier's
- b- positive and negative ions
- ☒ d- answer (b) and (c)
- c- No majority carrier's
- e- Neither (a), (b), nor (c)

6- If you are checking a 50 Hz full-wave bridge rectifier and observe that the output has a 50 Hz ripple


- a- the circuit is working properly
- ☒ b- there is an open diode
- c- the transformer secondary is shorted
- d- the filter capacitor is leakage

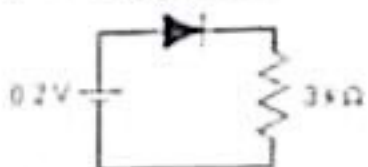7- Determine the voltage across the resistor $3 \text{ k}\Omega$.




- ☒ a- 0 V
- b- 0.9V
- c- 0.2V
- d- 0.44V

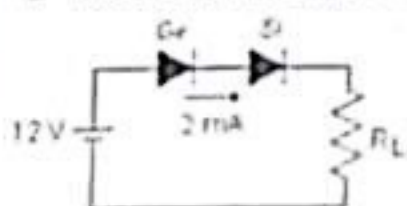8- Determine the value of the load resistor.



- a- $5 \text{ k}\Omega$
- b- $6 \text{ k}\Omega$
- ☒ c- $5.5 \text{ k}\Omega$
- d- $11 \text{ k}\Omega$

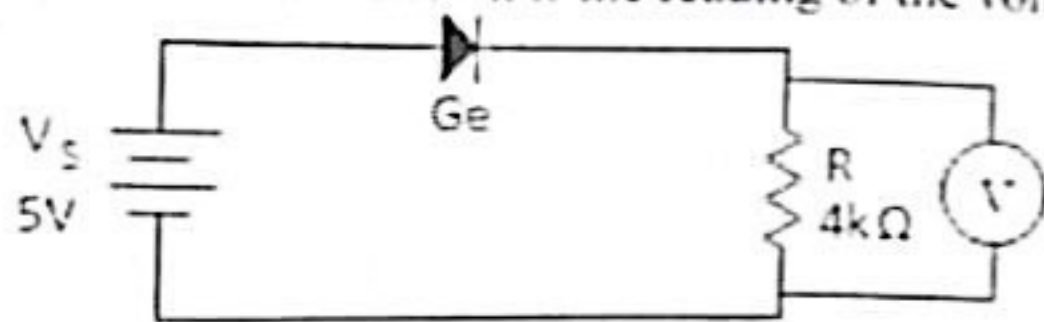9- for the circuit shown if the reading of the voltmeter is 5 V so the diode is:




a- in normal operation

b- open

☒ c- short

d- cannot be determined

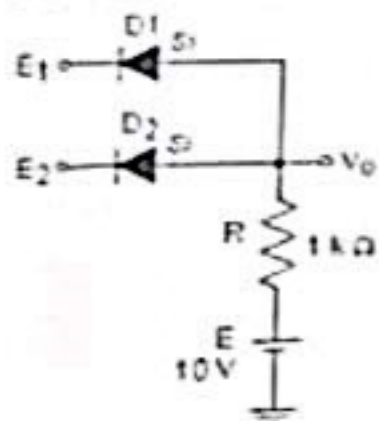10- Determine the current through each diode if $E_1 = E_2 = 0$ V.




a-0.7 mA

☒ b-4.65 mA

c-9.3 mA

d-18.6 mA

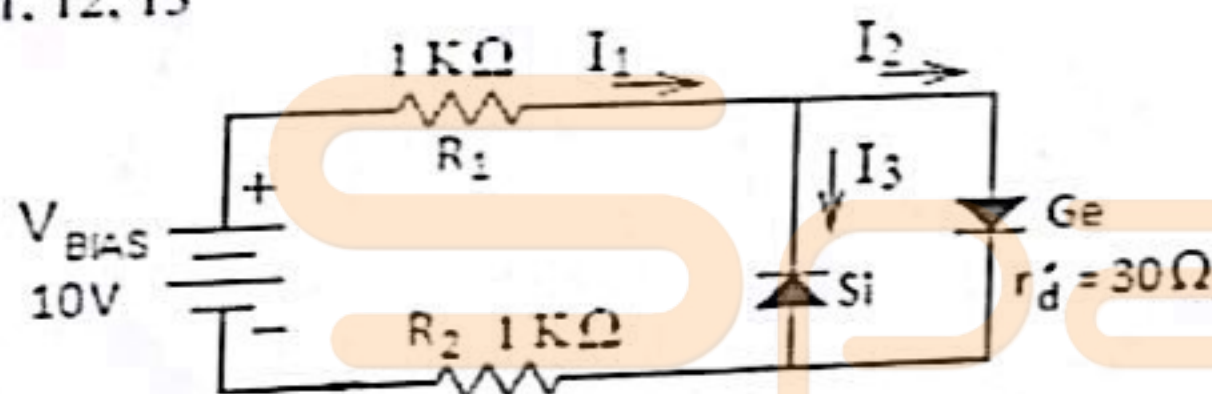11, 12, 13- for the circuit shown, assume that both diodes are complete piecewise (including r_d). Answer questions 11, 12, 13



11- the value of the current I_1 equal

a-0 mA

☒ b-4.78 mA

c-5.58 mA

d-4.65 mA

e- 5 mA

12- the value of I_2 equal

a-0 mA

☒ b-4.78 mA

c-5.58 mA

d-4.65 mA

e- 5 mA

13- the value of I_3 equal

☒ a-0 mA


b-4.78 mA

c-5.58 mA

d-4.65 mA

e- 5 mA

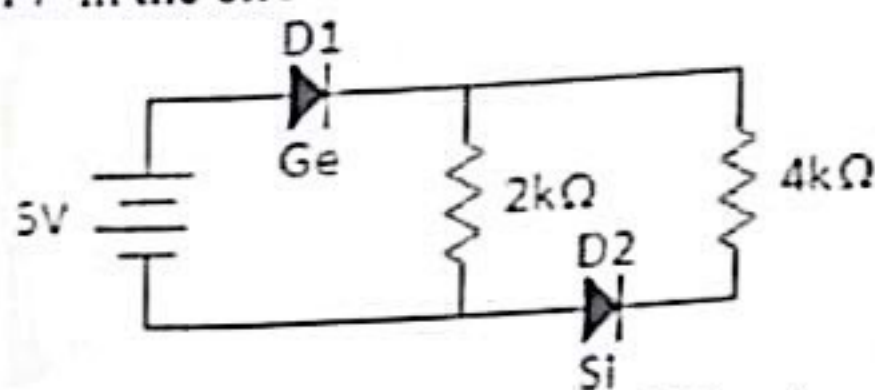14- in the circuit below the value of the current through the resistor 4 kΩ equal



☒ a-0 mA

b-1.075 mA

c-1 mA

d-1.25 mA

15- the voltage across D2 in circuit question 14 is

a-0 V


b- 5V

☒ c-4.3 V

d-0.7 V

Correct Answer : 4.7

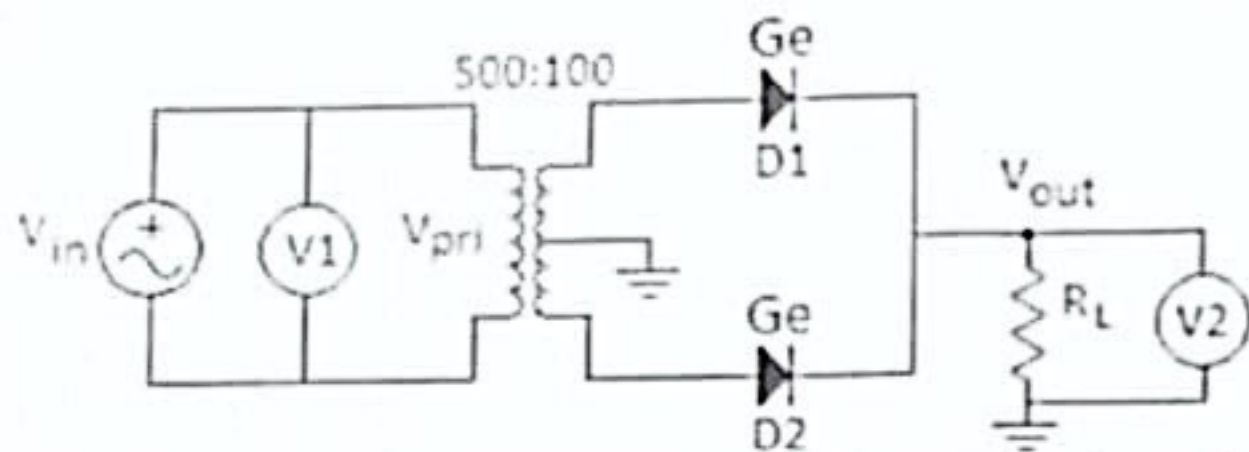* For the circuit shown answer the questions 16, 17, 18, 19, 20, 21



16- If the peak value of the output is ($V_{out} = 2.2 \text{ V}$) the reading of the voltmeter V2 is

- a-2.74 V **b- 1.4 V** c-0.68 V d-3.04 V

17- The maximum value of the secondary voltage (V_{sec}) equal to

- a-8.6 V **b- 15 V** c-5 V d-10 V

18- The maximum value of the primary voltage (V_{pri}) equal to

- a-5 V b- 35 V c-45 V **d- 25 V**


19- The reading of the voltmeter V1 is

- a-35.35 V **b- 17.68 V** c-42.43 V d-21.21 V

20- PIV for each diode is

- ~~a-10 V b- 6.2 V c-9.3 V d-4.7 V~~ Correct Answer: 9.7

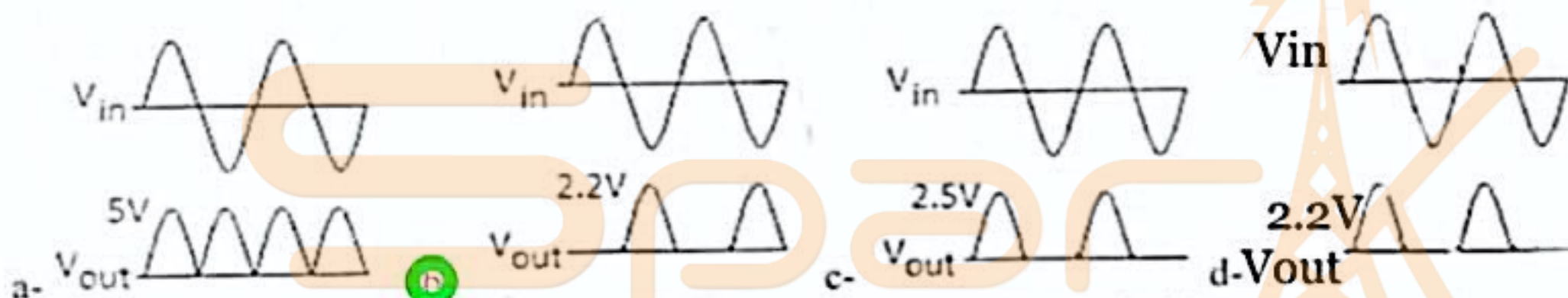21- If in the circuit the diode D1 is open so the output pulses will be




22- for practical zener diode in forward bias the voltage across its terminal is

- a- 0 V b- the applied voltage **c- 0.7 V** d- the Zener diode voltage

23- By addition of pentavalent to the silicon material the hole current is became

- a- Majority carrier **b- Minority Carrier** c- No change the hole current

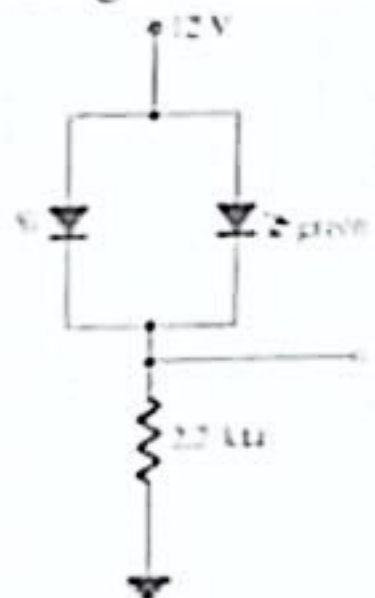24- For the circuit shown, if the forward voltage of the green diode is ($V_d = 2 \text{ V}$) the value of the current through the LED is



- a- 4.54 mA b- 5.136 mA c- 5.454 **d- 0 mA**




25- While making the test for the Zener diode circuit the output voltage received less than the Zener voltage in this case the Zener current is

- a- $I_Z = I_{Zmax}$ b- $I_Z = I_R$ c- $I_Z = I_L$ **$I_Z = 0 \text{ mA}$**

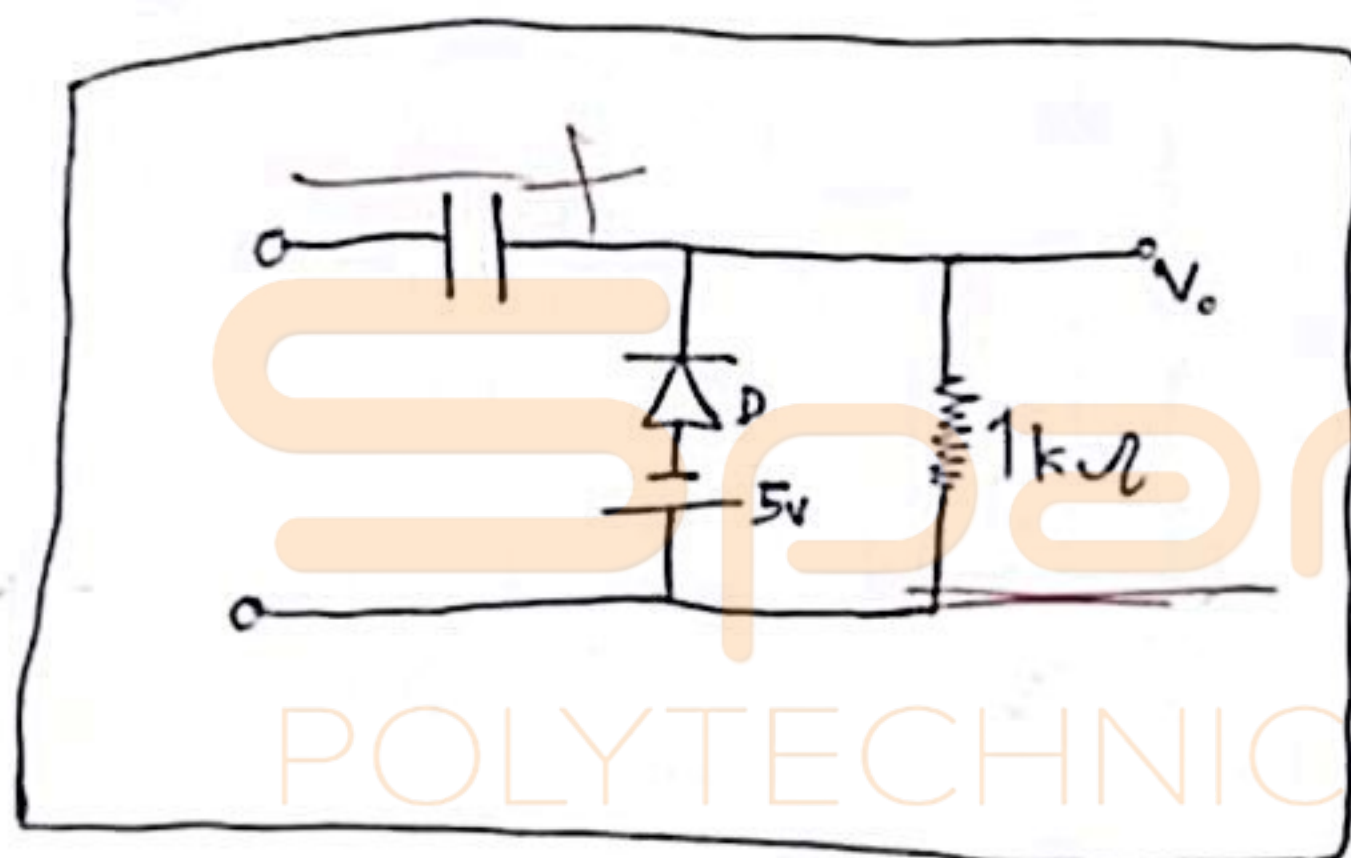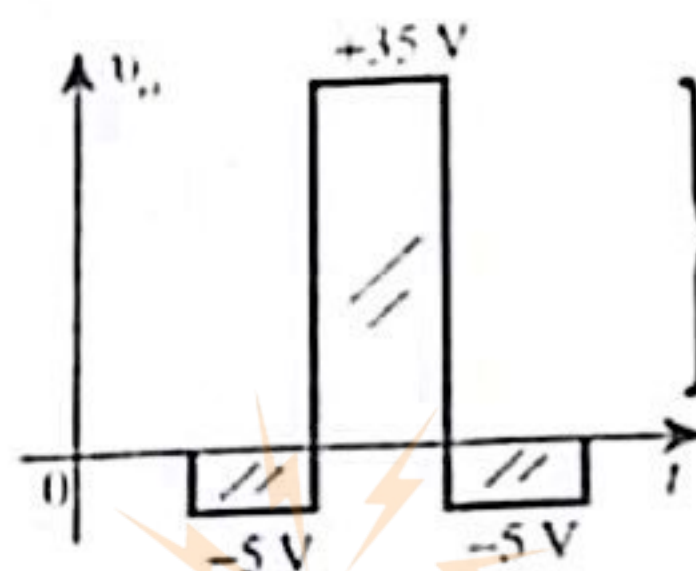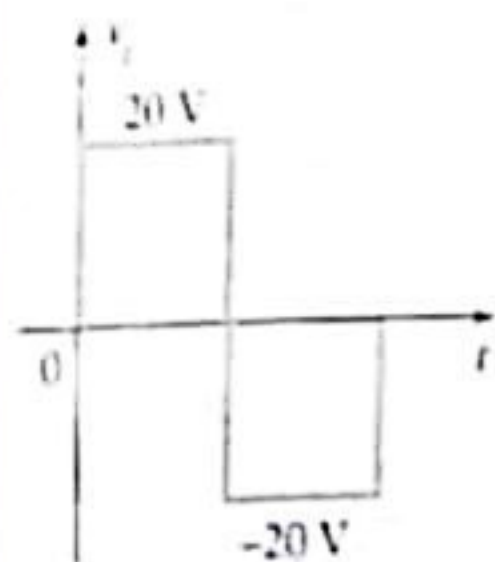Problem2

(5 points)

Design a clamper to perform the function indicated in figure shown (the diode in the circuit is ideal)



$$V_c = 15$$