

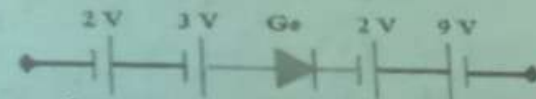


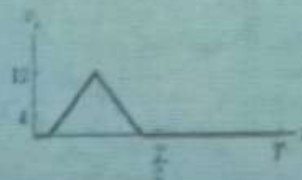
7. Gallium is considered as when added to the semiconductor.
 a. Acceptor atom b. Donor atom c. Both acceptor and donor d. Can not be determined.
8. For the following circuit, the status of the diode is (Assume a practical (simplified) model diode)
 a. Forward-biased b. Reverse-bias c. Breakdown region d. Not mentioned



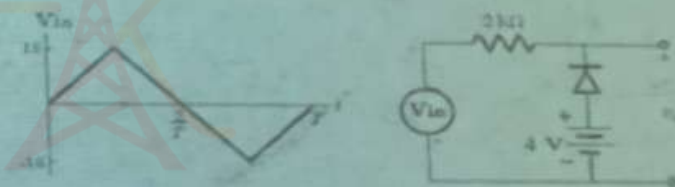
9. In a bridge configuration of full-wave rectifier and practical (simplified) model of Germanium (Ge) is used, the PIV for input voltage V_{in} is given as
 a. $V_m + 0.6V$ b. $V_m - 0.7V$ c. $V_m - 0.6V$ d. $V_m - 0.7V$ e. $V_m - 0.3V$ f. $V_m + 0.3V$
10. For the given circuit below with ideal diode is used, the expected output for the given input V_i is




a

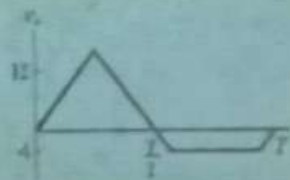

b

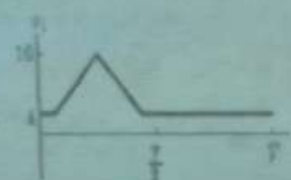

c

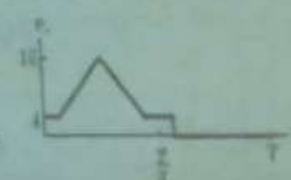

d

Q2. For the given circuit below, answer the following. Assume all the diodes are practical (simplified) model and the Zener diode is a Silicon diode. (4 Points)

Q2.1. For $V_{in} = 8\text{ V}$, find the value of V_L for $R_s = 0\ \Omega$.


***The main equation used to find V_L :

$$\dots - 8\text{ V} + 0.3\text{ V} + 0.3\text{ V} + V_L = 0$$

$$\text{or } 8\text{ V} - 0.3 - 0.3 - V_L = 0$$

***The value of V_L : Write the final answer only below

$$\dots V_L = 7.4\text{ V} \dots$$

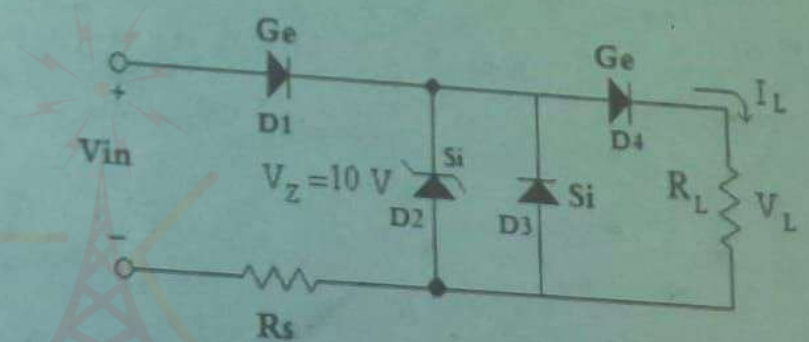

Q2.2. For $V_{in} = 15 \text{ V}$, determine the value of the current I_L for $R_L = 4.85 \text{ K}\Omega$ and $R_S = 100 \Omega$

***The main equation used to find I_L (Other than the Ohm's law equation):

$$\dots\dots\dots -10 \text{ V} + 0.3 \text{ V} + V_L = 0 \Rightarrow \dots\dots\dots \text{and } I_L = V_L / R_L \dots\dots\dots$$

Or $\dots\dots\dots 10 - 0.3 - V_L = 0$

***The value of I_L : Write the final answer only below

$$\dots\dots\dots I_L = 9.7 \text{ V} / 4.85 \text{ K}\Omega = 2 \text{ mA} \dots\dots\dots$$

