



Subject: Electronics 1
Duration: 50 min

Mid Exam

Spring 2025/2026

Q1: (a) In the circuit shown in the figure, find the diode voltage V_D and the supply voltage V such that the current is $I_D = 0.4 \text{ mA}$. Assume the diode threshold voltage is $V_T = 0.7 \text{ V}$. (b) Using the results of part (a), determine the power dissipated in the diode.

in KVL

in forward

(6 marks)

if I not zero

$$V_D = V_T = 0.7 \text{ V}$$

$$V_D = 0.7$$

not 0.0

$$-5 \text{ V} + (4.7 \text{ k}\Omega)(0.4 \text{ mA}) + 0.7 = 5 \text{ V}$$

$$7 \text{ V} = 0$$

$$V = 2.42 \text{ V}$$

+6

$$P_D = I_D \times V_D$$

$$= 0.4 \text{ mA} \times 0.7 \text{ V}$$

$$= 0.28 \text{ mW}$$


$$C.S.: V_D = 0.7 \text{ V}$$

$$I_D = I_R = I$$

in series

Q2: Assume each diode in the circuit shown in Figure has a threshold voltage of $V = 0.65 \text{ V}$. (a) The input voltage is $V_1 = 5 \text{ V}$. Determine the value of R_1 required such that I_{D1} is one-half the value of I_{D2} . What are the values of I_{D1} and I_{D2} ? (6 marks)

$$I_{D1} = \frac{1}{2} I_{D2}$$

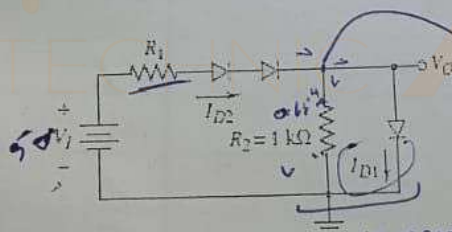

$$I_{in} = I_{out}$$

in parallel

$$V_R = V_D = 0.65 \text{ V}$$

$$I_{R2} = \frac{0.65}{1 \text{ k}\Omega}$$

$$= 0.65 \text{ mA}$$

$$I_{D2} = 0.65 \text{ mA} + I_{D1}$$


$$I_{D2} = 2(0.65 \text{ mA})$$

$$I_{D1} = 1.3 \text{ mA}$$


$$2 I_{D1} = 0.65 \text{ mA} + I_{D1}$$

$$I_{D1} = 0.65 \text{ mA}$$

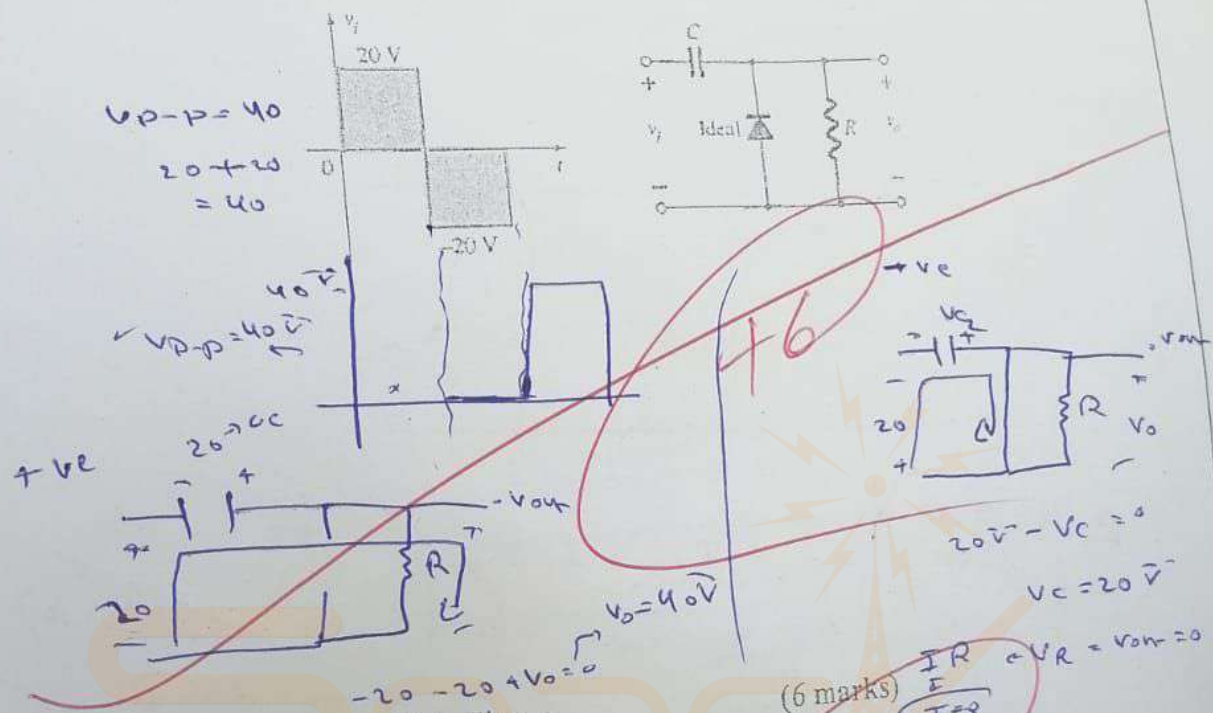
Q3: Sketch V_o for the network of Fig. for the input shown. (6 marks)



Q4: Sketch v_o for the circuit in Figure

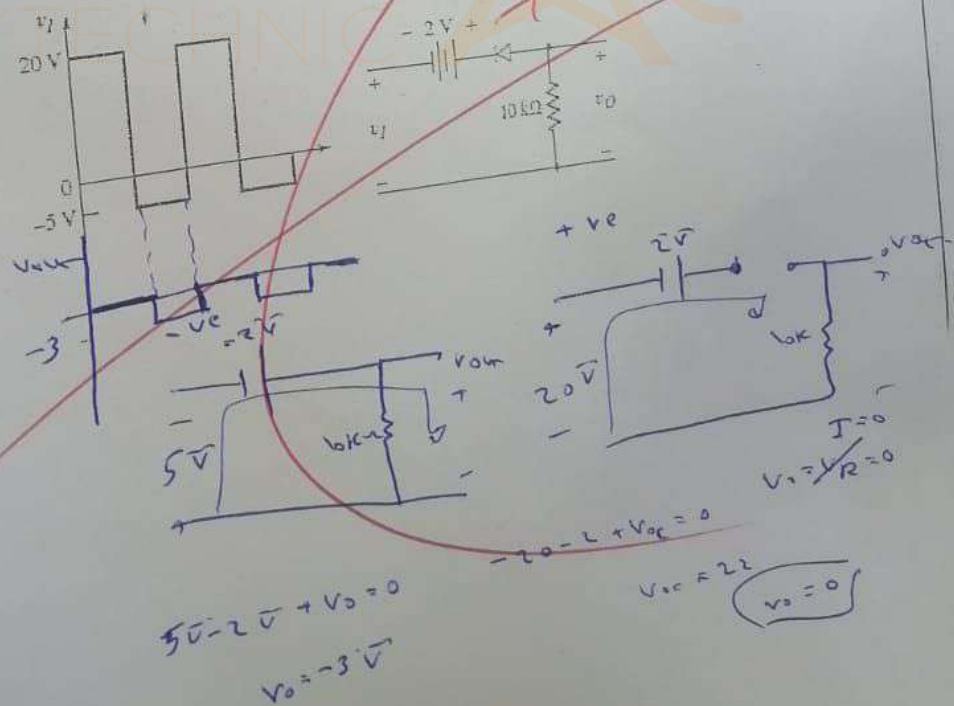

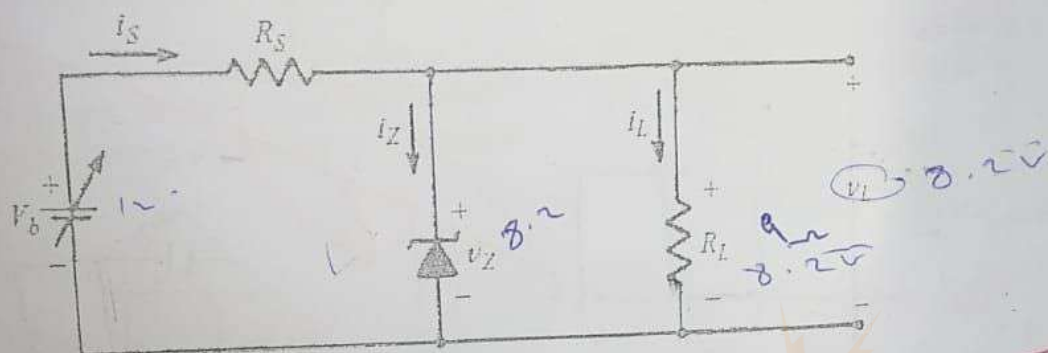Q5: The Zener diode in the voltage-regulator circuit of the following Fig. has a constant reverse breakdown $V_Z = 8.2\text{V}$, for $75\text{mA} \leq i_Z \leq 1\text{A}$. If $R_L = 9\Omega$, find R_S so that $v_L = V_Z$ is regulated to 8.2V while V_b varies by ± 10 percent from its nominal value of 12V . (6 marks)



$R_s = 3.85\Omega$
when $V_b = 12$

$I_{L \min} = I_s - I_{Z \max}$
 $I_L = \frac{V_L}{R_L} = \frac{8.2}{9} = 0.911\text{A}$

$I_s = \frac{V_{in} - V_Z}{R_s}$

$9.82\text{mA} = \frac{12 - 8.2}{R_s}$

$R_s = \frac{1.8}{0.986\text{mA}}$

when $R_s = 1.8255\Omega$
 $V_b = 10\text{V}$

$I_{Z \min} = 75\text{mA}$

$I_{L \max} + I_{Z \min} = I_s$

$I_s = 75\text{mA} + 911\text{mA}$

$I_s = 986\text{mA}$

$10 + V_s + 8.2 =$

$V_s = 1.8$

$R_s = \frac{1.8}{I_s - 986\text{mA}} = 1.825\Omega$