

Electronics lab
FINAL EXAM
2025-Second semester

Student name: _____

std. no.: _____

Q1: Choose the correct answer – fill the table at the end

1. The unit of I_B in a BJT is:
 - a) I_{mA}
 - b) $I_{\mu A}$
 - c) I_A
 - d) Watt

2. A FET is tested using a DMM, the resistance from gate to source should be:
 - a) very Low resistance
 - b) Zero
 - c) very high resistance
 - d) not mentioned

3. In a Half-Wave Rectifier (HWR), the output frequency observed on the oscilloscope is:
 - a) Same as input
 - b) Half of input
 - c) Double the input
 - d) Quarter of input

4. In Fixed Bias BJT, the input characteristic curve is:
 - a) V_{BE} vs I_B for different V_{CB} values
 - b) V_{BE} vs I_B for different V_{CB} values
 - c) V_{CE} vs I_C for different I_B values
 - d) V_{CE} vs I_C for different V_B values

5. In diode characteristics, when the voltage exceeds point A for a normal diode is....._,and for a zener is :
 - a) damaged/working
 - b) working/damaged
 - c) damaged/damaged
 - d) working/working

6. For a clamper circuit, if the output voltage = 15v peak voltage, then the V_{rms} is:
 - a) 15V
 - b) 10.6
 - c) 5
 - d) 21.21v


7. In a rectifier circuit, increased ripple means:
- More effective filtering with higher DC voltage
 - More effective filtering with less DC voltage
 - less effective filtering with higher DC voltage
 - less effective filtering with lower DC voltage

8. While using a fully functional DMM to test a BJT, with the positive to B and negative to C, the reading will be:

- 0v
- O.L (over load)
- around 0.7v
- not determined

9. Find the voltage across point a,b For the positive half cycle, not that the diode is a silicone diode

- 7V
- +12V
- 0V
- 12V

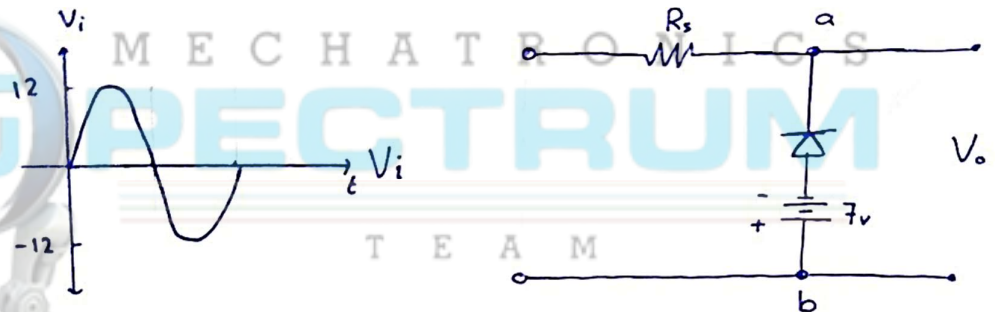


10. For the same circuit, If the Resistance = $2k\Omega$ and the diode is ideal, then the current through the resistor equals:

- 0A
- 0.35 mA
- 1 mA
- 2.5 mA

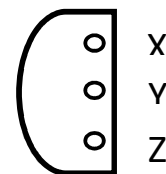11. For a JFET, from bottom view, the pins X-Y-Z are:

- Source - Gate - Drain
- Gate - Source - Drain
- Drain - Source - Gate
- Gate - Drain - Source




12. In the BJT experiment, the current gain/amplification for a common base is, and for a common emitter is.....

- I_c / I_b , I_c / I_b
- I_e / I_b , I_c / I_b
- I_c / I_b , I_e / I_b
- I_c / I_b , I_c / I_e

13. For the given clamper circuit, with ideal diode, the voltage of the capacitor is:

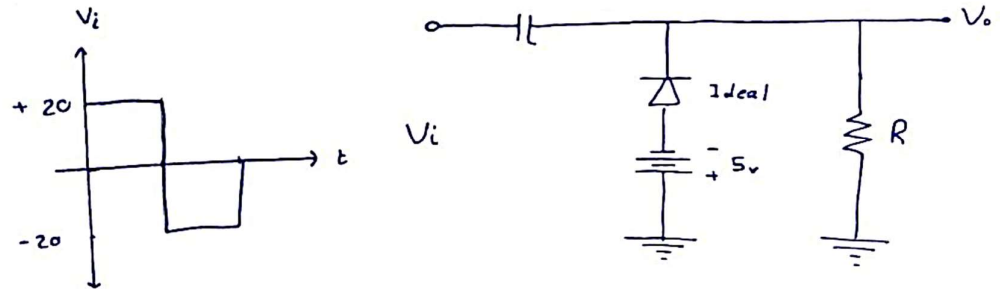- a) +15v
- b) +14.3v
- c) +20v
- d) not mentioned



14. The FET transistor compared to the BJT is a..... with.....


- a) Voltage controlled device and a high input resistance
- b) Voltage controlled device and a low input resistance
- c) current controlled device and a low input resistance
- d) current controlled device and a high input resistance

15. For a n-type FET characteristics curve is drawn for a values of V_{GS}

- a) positive
- b) negative
- c) variable
- d) not mentioned

16. For the given circuit, the BJT configuration is: __

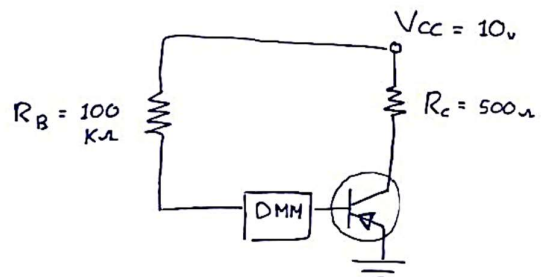
- a) common base
- b) common emitter
- c) fixed biased
- d) not mentioned



17. for the same circuit If the current gain was 100, and the current through resistor C is 9.3 mA then the reading of the DMM will be:

- a) 93 μ A
- b) 68 μ A
- c) not determined
- d) 0 mA

For the given circuit, answer 18,19,20

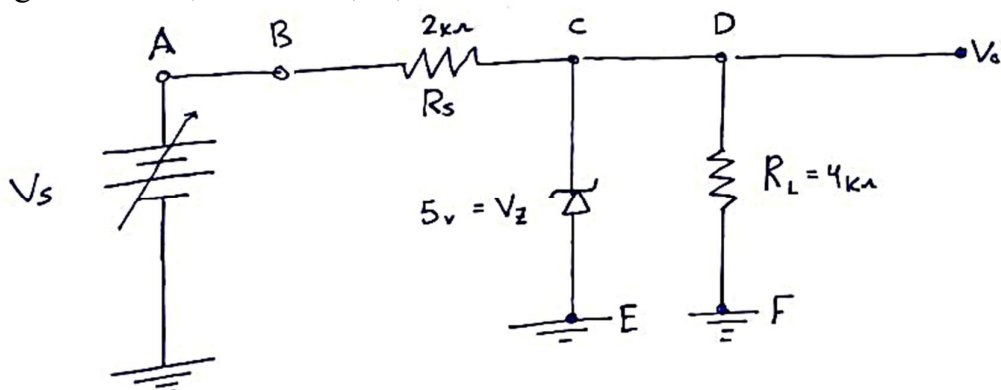

18. If $V_s=4\text{v}$, then the reading of the DMM between terminals A and B is:

- a) 0 mA
- b) 0.5 mA
- c) 1.3 mA
- d) not determined

19. If $V_s=8\text{v}$, then the reading of the DMM on the R_s is:


- a) 1.5 mA
- b) 3 v
- c) 13 v
- d) 5.5 v

20. If $V_s=10\text{v}$, then the reading of the DMM between terminals C and D is::

- a) 5v
- b) 1.25 v
- c) 2.5 mA
- d) not mentioned

1	2	3	4	5	6	7	8	9	10
					T	E	A	M	
11	12	13	14	15	16	17	18	19	20

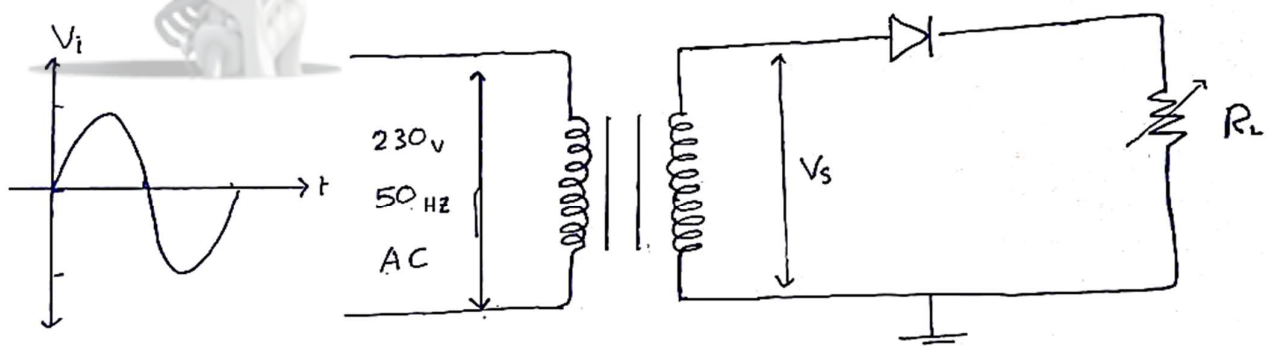Question 2 : Given the circuit below, answer the following questions:



Q2.1) What is the name and objective of the given circuit?

Q2.2) What is the effect of adding a capacitor to the circuit?

Q2.3) Based on your answer in Q2.2, what is the effect of increasing the load resistor from $2\text{ k}\Omega$ to $10\text{ k}\Omega$?

Q2.4) Explain how to measure the AC current through using only a Digital Multimeter (DMM).

Q2.5) Assume we connected an oscilloscope in parallel with R_L . If the output frequency is 6 kHz , what would be the expected input frequency?



MECHATRONICS
SPECTRUM
TEAM

End.