


PLC

Timer and Counter Example

Write a logic ladder diagram to implement the following process using a PLC.

1. Start push-Button is used to start the process and a stop push-Button is used to stop the process.
2. A proximity switch is used to detect moving objects on the conveyor belt 1.
3. Another proximity switch is used to detect an empty box on conveyor belt 2.
4. 6 objects should be placed in every box.
5. When number of objects to be packed are detected timer is activated the time between the moving of empty boxes is set to be 2 sec. When time is over, it moves the conveyor belt 2 until next empty box is detected.


Problem Diagram

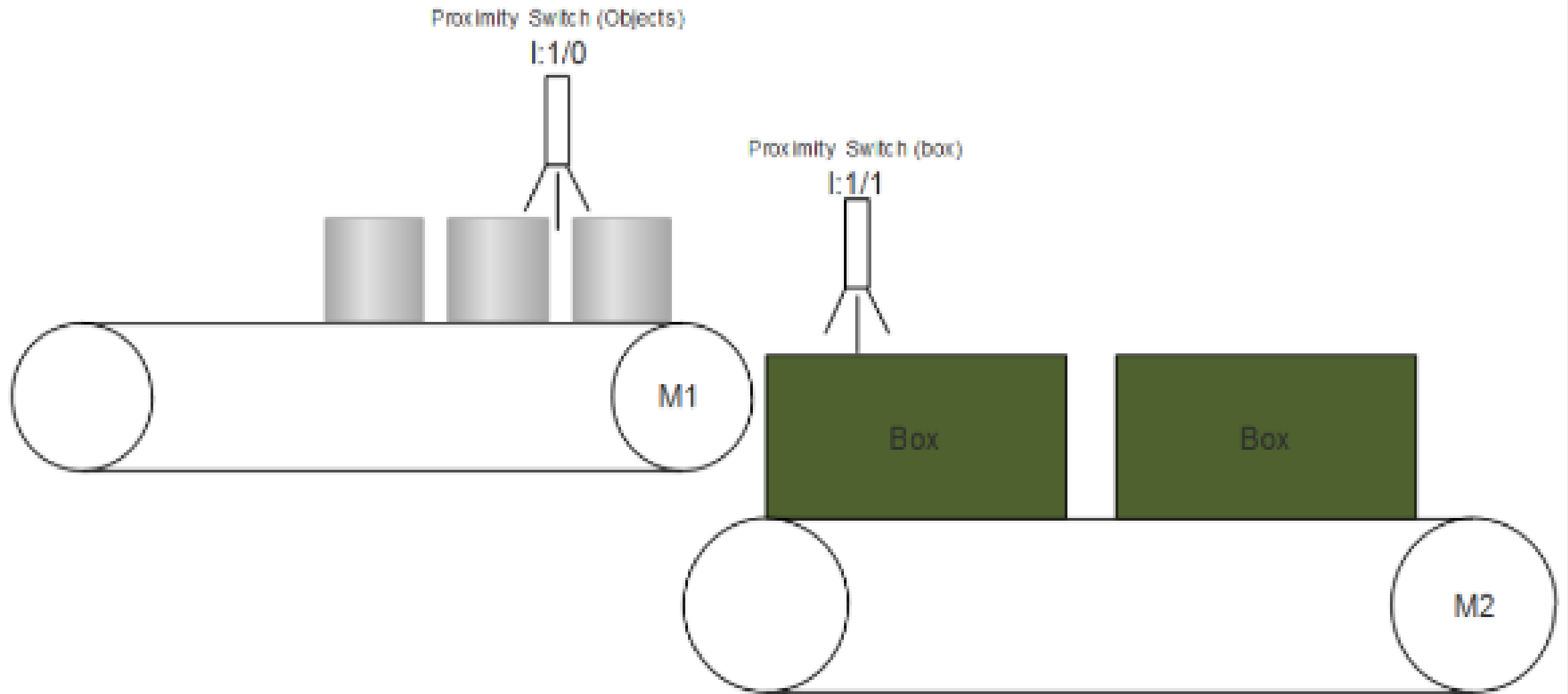

PLC Program

List of Inputs and Outputs

I:1/14	= Start	(Input)
I:1/15	= Stop	(Input)
B3:0/0	= Latching Bit	(Bit)
B3:0/1	= Latching Motor 1 bit	(Bit)
I:1/0	= Part detection	(Input)
I:1:1	= Box detection	(Input)
O:2/0	= Conveyor Belt 1	(Output)
O:2/1	= Conveyo2 Belt 2	(Output)
C5:0	= Part counter	(Counter)
T4:0	= Timer to stop conveyor	(Timer)

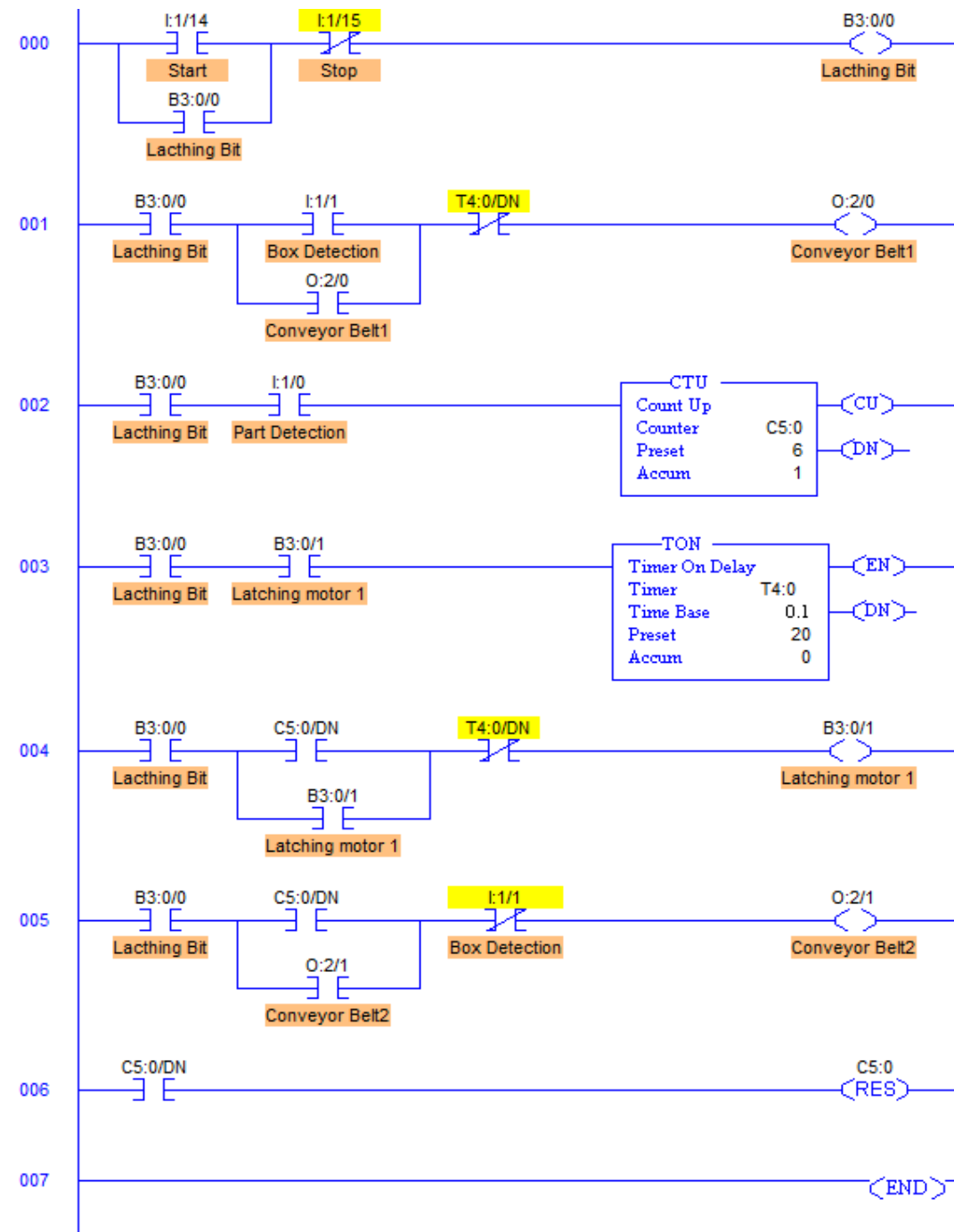

Program Description

- RUNG000 is for master start and stop the process.
- RUNG001 is for controlling Conveyor Belt 1 motor M1 which is operated by Box Detection proximity switch. When the process is started and empty box is detected by Proximity having address of I:1/1, power supply to the motor of Conveyor Belt 1 is given. This drives the Motor M1 moving objects on the conveyor belt 1.
- Every time a part is detected by the I:1/1 Part detector, Counter C5:0 is incremented by 1. Counter has a preset value of 6, counter done bit C5:0/DN is set to 1.
- When C5:0/DN bit is set, timer T4:0 is activated for 2secs which is an assumption that the part will take approximately 2secs to fall into the box after it is detected by the Pat Detector proximity switch I:1/0.
- Counter is immediately reset when C5:0/DN goes true. So one shot is generated by C5:0/DN bit.
- Conveyor Belt 2 motor M2 (O:2/1) is operated when counter value reaches to 6.
- And the process is repeated.

PLC Program to Drive Motors Simultaneously with Interlocking

Problem Description


Two Motors are running in a sequence one by one for a particular time. If the start button is pressed Motors run in sequence such that 1st Motor stays ON for 5secs and then 2nd Motor is turned ON and stays ON for 5secs. And the cycle is repeated until it is interrupted. While motors are running in the sequence, if one motor is running and the button of other motor is pressed, then the running Motor should stop and the other motor should run. Implement this logic in PLC using Ladder Diagram programming language.


Problem Solution

- Define addresses of motors.
- Use pushbuttons to start and stop the sequential operation.
- Use TON timer to generate a particular time delay.
- Use the enable bit of first timer to energize 2nd motor coil and activate second timer.
- No need to use Reset contact, program will reset the timers itself after completion of each cycles.
- Use Parallel Start Motor contact to start one motor when other motor is running.

PLC Program

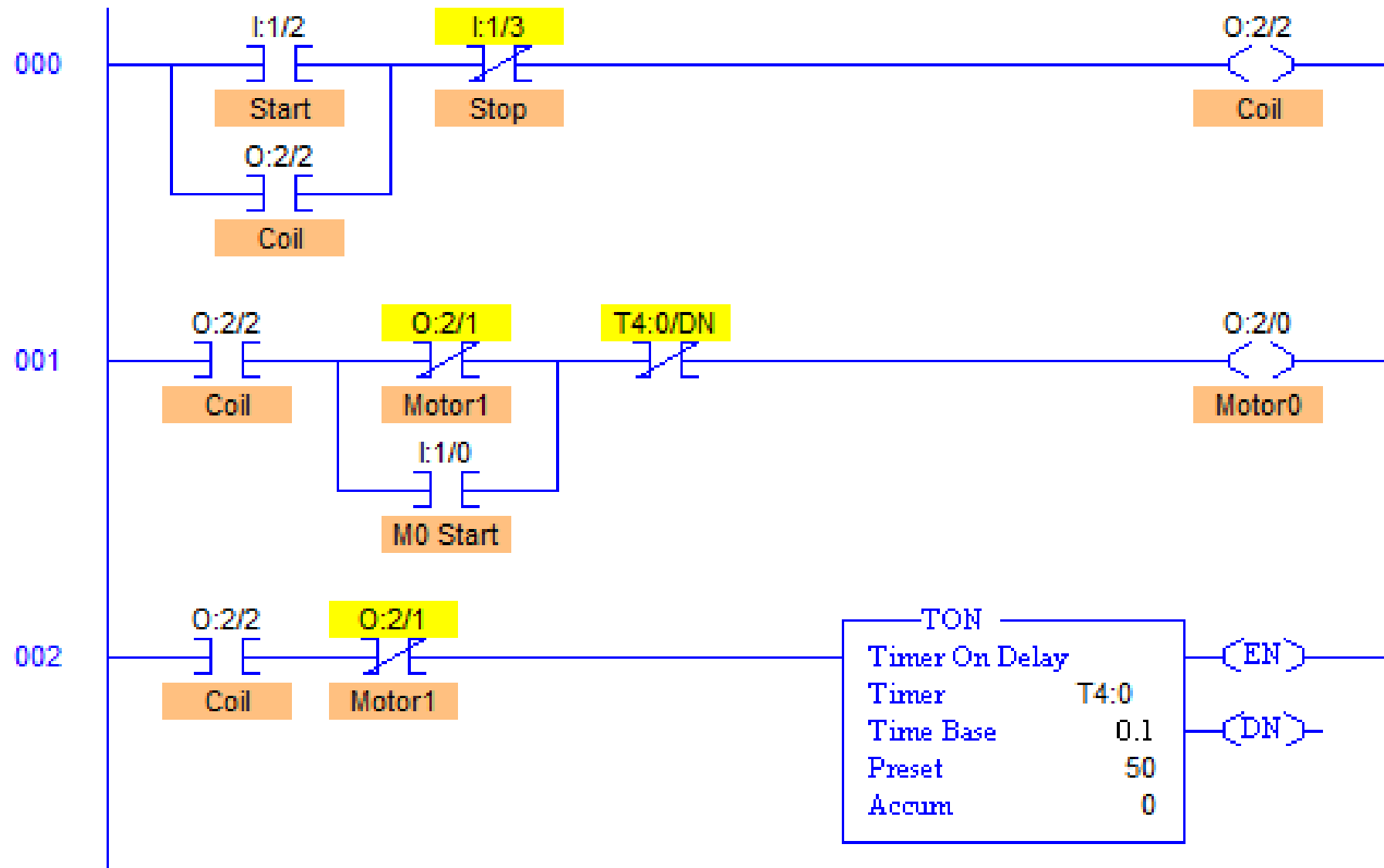- List of Inputs and Outputs
- I:1/0 = Motor 0 Start (Input)
- I:1/1 = Motor 1 Stop (Input)
- I:1/2 = Master Start (Input)
- I:1/3 = Master Stop (Input)
- O:2/2 = Master Coil (Output)
- O:2/0 = Motor 0 (Output)
- T4:0 = Motor 0 Timer (Timer)
- O:2/1 = Motor 1 (Output)
- T4:1 = Motor 1 Timer (Timer)



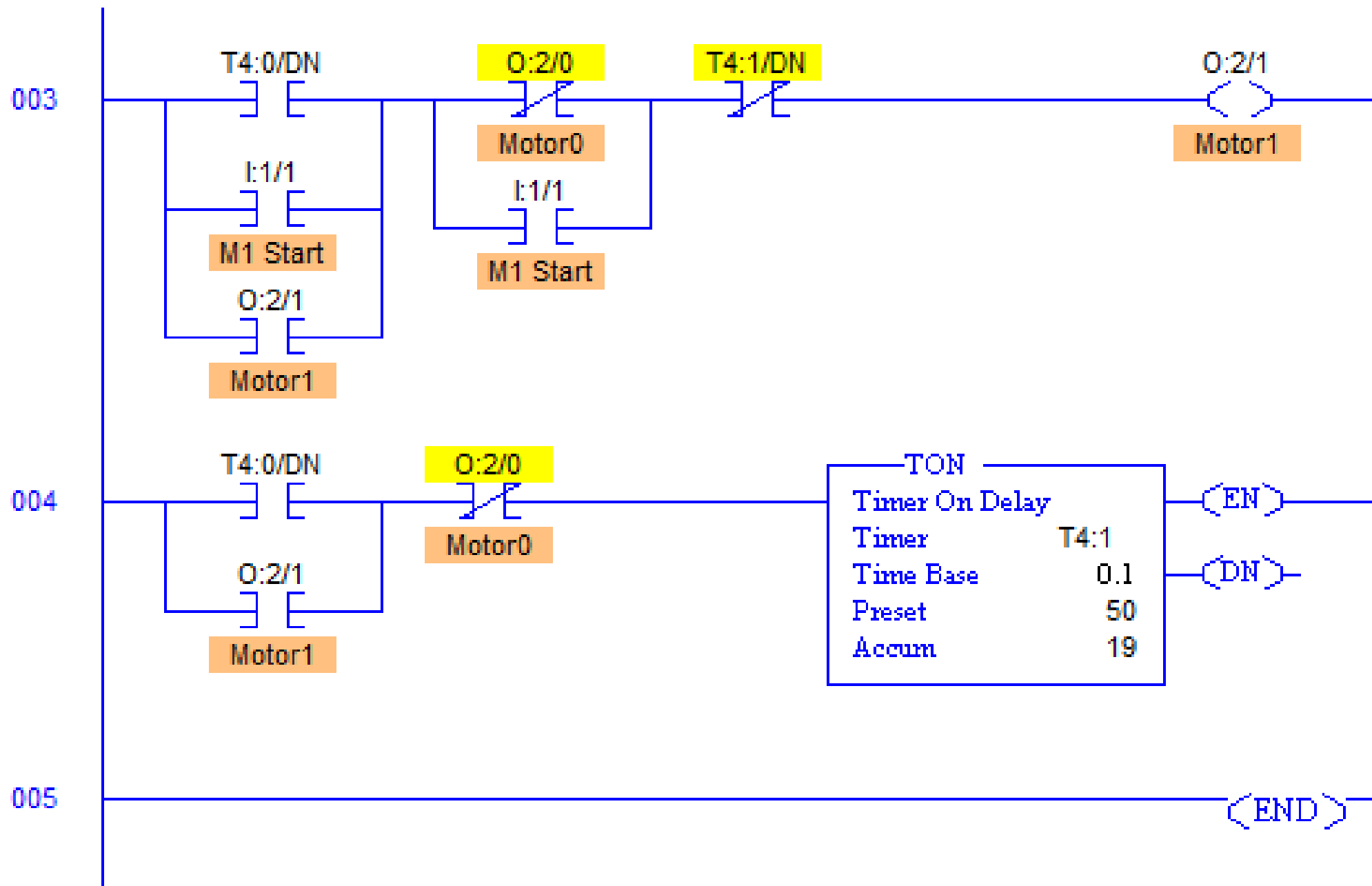

Program Description

- RUNG000 is Latching coil for Master Start and Stop.
- RUNG001-RUNG002 and RUNG003-RUNG004 are arrangements to operate Motor0 O:2/0 and Motor1 O:2/1 respectively.
- When Start button is pressed momentarily, it latches the coil starting the energizing the output O:2/0, hence turning Motor0 ON.
- Timer T4:0 is used to run Motor0 for 5secs (Less because of simulation purpose).
- Similarly T4:1 is used to run Motor1 for 5secs.

- While Motor0 is running, and M1 Start I:1/1 is pressed, it stops the Motor0 (O:2/0 de-energizes) and Motor1 (O:2/1 energizes) starts and timer t4:1 is activated. And vice-versa.
- XIO contact of each motor's output is used to turn other motor off by de-energizing other motor's output which cuts off the current supply in the field.

PLC Example

Traffic lights


Control of a set of traffic lights in one direction

Operation of the program:

- Transition from red light to green light to amber light is accomplished by the interconnection of the three TON timer instructions.
- The input to timer T4:0 is controlled by the T4:2 done bit.
- The input to timer T4:1 is controlled by the T4:0 done bit.
- The input rung to timer T4:2 is controlled by the T4:1 done bit.

- The timed sequence of the lights is:
- Red—30 s on
- Green—25 s on
- Amber—5 s on

The sequence then repeats itself.

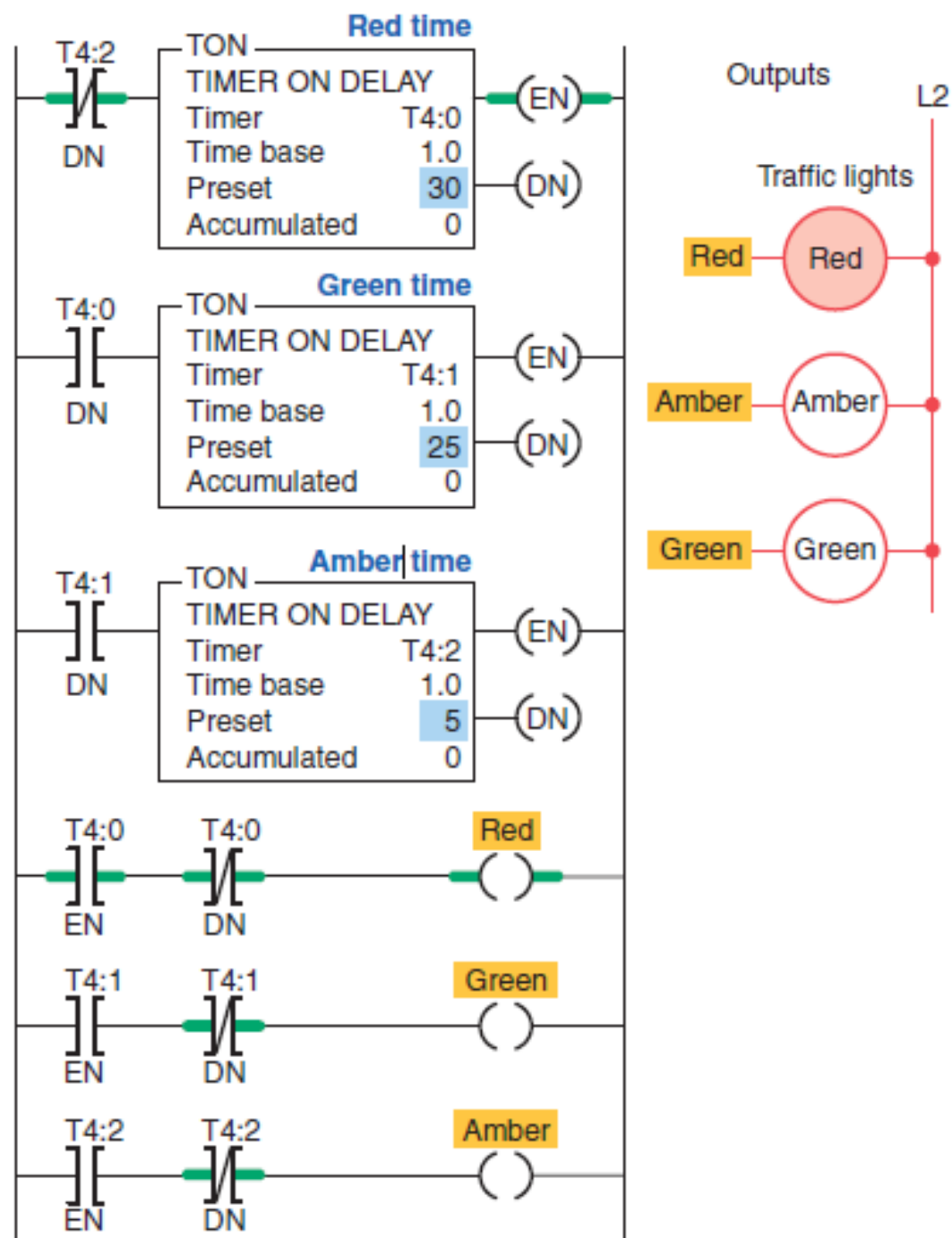

Control of a set of traffic lights in two direction

