

Half wave

$$\rightarrow V_{dc} = \frac{V_m}{\pi}$$

$$\rightarrow I_{dc} = \frac{V_m}{\pi R}$$

$$\rightarrow V_{rms} = \frac{V_m}{2}$$

$$\rightarrow I_{rms} = \frac{V_m}{2R}$$

$$\rightarrow P_{dc} = \frac{V_m^2}{\pi^2 R}$$

$$\rightarrow P_{ac} = \frac{V_m^2}{4R}$$

$$\rightarrow \eta = 40.5\%$$

$$\rightarrow R.F = \frac{V_{RI}(V_{ac})}{V_{dc}} = 1.2114$$

$$\rightarrow F.F = \frac{V_{rms}}{V_{dc}} = 1.5707$$

$$\rightarrow V_{RI} = V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

Full wave

$$\rightarrow V_{dc} = \frac{2V_m}{\pi}$$

$$\rightarrow I_{dc} = \frac{2V_m}{\pi R}$$

$$\rightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\rightarrow I_{rms} = \frac{V_m}{\sqrt{2} R}$$

$$\rightarrow P_{dc} = \frac{4 V_m^2}{\pi^2 R}$$

$$\rightarrow P_{ac} = \frac{V_m^2}{2R}$$

$$\rightarrow \eta = 81.05\%$$

$$\rightarrow R.F = 0.48343$$

$$\rightarrow F.F = 1.1107$$

controlled

with α

Single - phase

Half wave

$$\rightarrow V_{dc} = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$\rightarrow I_{dc} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

$$\rightarrow V_{rms} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

$$\rightarrow I_{rms} = \frac{V_m}{2R} \sqrt{\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

$$\rightarrow P_{ac} = \frac{V_{rms}^2}{R}$$

$$\rightarrow P_{dc} = \frac{V_{dc}^2}{R}$$

Full wave

$$\rightarrow V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$\rightarrow I_{dc} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$

$$\rightarrow V_{rms} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}}$$

$$\rightarrow I_{rms} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin 2\alpha}{4\pi}}$$

$$\rightarrow P_{ac} = \frac{V_{rms}^2}{R}$$

$$\rightarrow P_{dc} = \frac{V_{dc}^2}{R}$$

* Single - phase half wave : (1 pulse)

* Single - phase full wave : (2 pulse)

uncontrolled

Three-phase

Half wave

$$\rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{2\pi}$$

$$\rightarrow I_{dc} = \frac{3\sqrt{3} V_m}{2\pi R}$$

$$\rightarrow V_{rms} = 0.84 \cdot V_m$$

$$\rightarrow I_{rms} = \frac{0.84 V_m}{R}$$

$$\rightarrow P_{dc} = \frac{27 V_m^2}{4\pi^2 R}$$

$$\rightarrow P_{ac} = \frac{0.7056 V_m^2}{R}$$

Full wave

$$\rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{\pi}$$

$$\rightarrow I_{dc} = \frac{3\sqrt{3} V_m}{\pi R}$$

$$\rightarrow V_{rms} = 1.655 V_m$$

$$\rightarrow I_{rms} = 0.78 I_m \text{ (phase)}$$

$$\rightarrow I_{rms} = 0.552 I_m \text{ (diode)}$$

$$\rightarrow I_m = \frac{1.73 V_m}{R}$$

$$\rightarrow P_{dc} = \frac{27 V_m^2}{\pi^2 R}$$

$$\rightarrow P_{ac} = \frac{1.29 V_m^2}{R}$$

Controlled

with α

Three-phase

Half wave

when $\alpha \leq 30^\circ$

$$\rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{2\pi} \cos \alpha$$

$$\rightarrow I_{dc} = \frac{3\sqrt{3} V_m}{2\pi R} \cos \alpha$$

$$\rightarrow V_{rms} = \sqrt{3} V_m \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

$$\rightarrow I_{rms} = \frac{\sqrt{3} V_m}{R} \sqrt{\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha}$$

Full wave

when $\alpha \leq 30^\circ$

$$\rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{\pi} \cos \alpha$$

$$\rightarrow I_{dc} = \frac{3\sqrt{3} V_m}{\pi R} \cos \alpha$$

$$\rightarrow V_{rms} = \sqrt{3} V_m \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

$$\rightarrow I_{rms} = \frac{\sqrt{3} V_m}{R} \sqrt{\frac{1}{2} + \frac{3\sqrt{3}}{4\pi} \cos 2\alpha}$$

when $\alpha \geq 30^\circ$

$$\rightarrow V_{dc} = \frac{3V_m}{2\pi} \left(1 + \cos \left(\frac{\pi}{6} + \alpha \right) \right)$$

$$\rightarrow I_{dc} = \frac{3V_m}{2\pi R} \left(1 + \cos \left(\frac{\pi}{6} + \alpha \right) \right)$$

$$\rightarrow V_{rms} = V_m \sqrt{\frac{3}{4\pi} \left[\frac{5\pi}{6} - \alpha + \frac{1}{2} \sin \left(\frac{\pi}{3} + 2\alpha \right) \right]}$$

$$\rightarrow I_{rms} = \frac{V_m}{R} \sqrt{\frac{3}{4\pi} \left[\frac{5\pi}{6} - \alpha + \frac{1}{2} \sin \left(\frac{\pi}{3} + 2\alpha \right) \right]}$$

when $\alpha > 60^\circ$

$$\rightarrow V_{dc} = \frac{3\sqrt{3} V_m}{\pi} \cos \left(\frac{\pi}{3} + \alpha \right)$$

$$\rightarrow I_{dc} = \frac{3\sqrt{3} V_m}{\pi R} \cos \left(\frac{\pi}{3} + \alpha \right)$$

* Three-phase Half wave : (3 pulse)

* Three-phase Full wave : (6 pulse)